
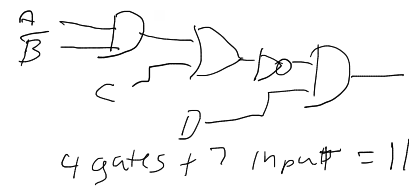


Demorgan's

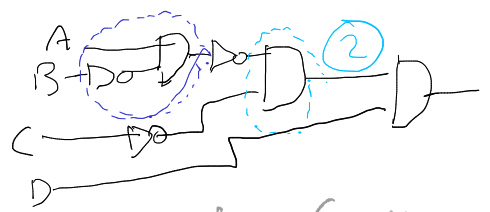$X+Y = \overline{\overline{X} \cdot \overline{Y}}$



Boolean Algebra for Synthesis

1 $f = \overline{A \cdot B} + C \cdot D$

get rid of "big bars"


2 $\overline{A \cdot B} \cdot \overline{C} \cdot D$

3 $(\overline{A} + \overline{B}) \cdot \overline{C} \cdot D$

Distributive law

$f = \overline{A} \overline{C} D + \overline{B} \overline{C} D$

SOP
Sum of Products

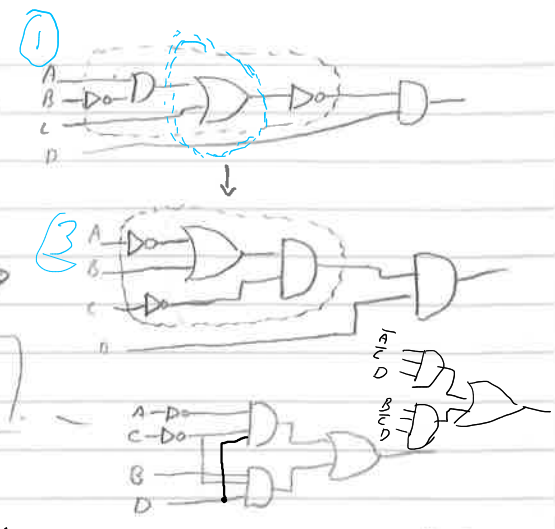

* Also use Boolean Algebra

$\overline{A} \overline{C} D (B + \overline{B}) + \overline{B} \overline{C} D (A + \overline{A})$
 $\overline{A} \overline{B} \overline{C} D + \overline{A} B \overline{C} D + A \overline{B} \overline{C} D + \overline{A} \overline{B} C D$

canonical minterm form

$f = \overline{A} \overline{B} \overline{C} D + \overline{A} B \overline{C} D + A \overline{B} \overline{C} D$
 $f = m_1 + m_5 + m_{13}$

do this for SOP also

one measure

of cost = # gates + # inputs to all gates (include inverters)

$\overline{A} \overline{B} C = m_5$

Original circuit cost = 4
 SOP cost = 14
 canonical cost = 25

ABCD	f	A+B+C+D	A+B+C+D
0000	0	0	1
0001	1	1	1
0010	0	1	0
0011	0	1	1
0100	0	1	1
0101	1	1	1
0110	0	1	1
0111	0	1	1
1000	0	1	1
1001	0	1	1
1010	0	1	1
1011	0	1	1
1100	0	1	1
1101	1	1	1
1110	0	1	1
1111	0	1	1


maxterm form $f = \prod M(0, 2, 3, 4, 6, 7, 8, 9, 10, 11, 12, 14, 15)$

$(A+B+C+D) f = (A+B+C+D)(A+B+\overline{C}+\overline{D})(A+B+\overline{C}+D)(A+\overline{B}+C+D)(A+\overline{B}+\overline{C}+D)$
 $(A+\overline{B}+\overline{C}+\overline{D})(\overline{A}+B+C+D)(\overline{A}+B+\overline{C}+D)(\overline{A}+\overline{B}+C+D)(\overline{A}+\overline{B}+\overline{C}+D)$

$(x+y)(x+\overline{y}) = x$
 $(\overline{A}+\overline{B}) \overline{C} D$

* $f = (\overline{A} + \overline{B}) \overline{C} D$ ← this is POS.

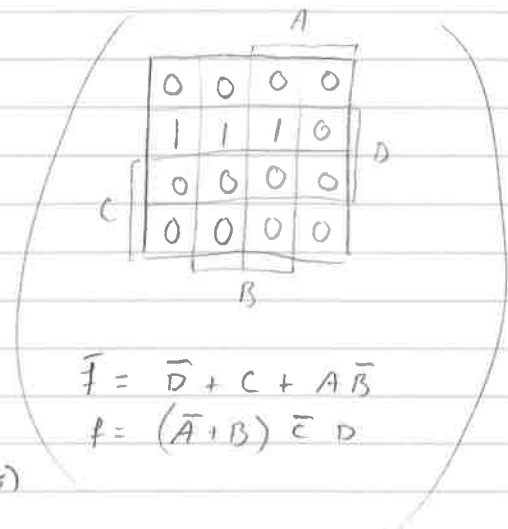easy to get this from SOP using algebraic manipulation



$\overline{f} = \overline{D} + C + A \overline{B}$
 $f = (\overline{A} + \overline{B}) \overline{C} D$

Note \overline{f} = complement of f (in truth table)

minterms of \overline{f} = maxterms of f
 treat zeros of f as ones (this is \overline{f})

Demorgan's



$\overline{f} = \overline{A \overline{B} + C + \overline{D}}$
 $\overline{f} = (\overline{A} + B) \cdot \overline{C} \cdot D$
 $f = (\overline{A} + B) \cdot \overline{C} \cdot D$

Also maxterms
 $\overline{f} = \sum m(0, 2, 3, 4, 6, 7, 8, 9, 10, 11, 12, 14, 15)$
 $= \overline{A} \overline{B} \overline{C} D + \overline{A} B \overline{C} D + \dots$
 $f = (A+B+C+D)(A+B+\overline{C}+\overline{D}) \dots$

multiple ways to solve

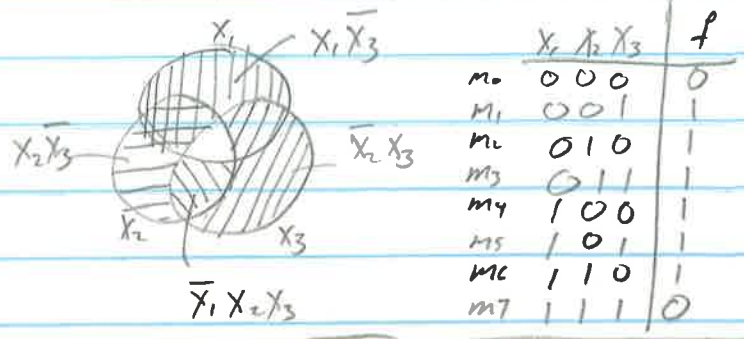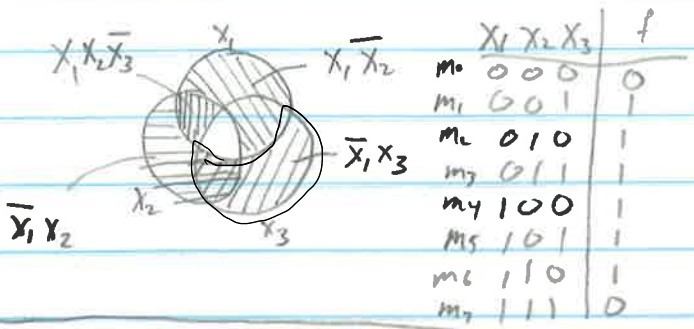2.7a in text

$$\bar{X}_1 X_3 + X_1 X_2 \bar{X}_3 + \bar{X}_1 X_2 + X_1 \bar{X}_2 = \bar{X}_2 X_3 + X_1 \bar{X}_3 + X_2 \bar{X}_3 + \bar{X}_1 X_2 X_3$$



$$\bar{X}_1 X_3 + X_1 X_2 \bar{X}_3 + \bar{X}_1 X_2 + X_1 \bar{X}_2$$

$$\bar{X}_1 \bar{X}_2 X_3 + \bar{X}_1 X_2 X_3 + X_1 \bar{X}_2 \bar{X}_3 + \bar{X}_1 X_2 \bar{X}_3 + X_1 X_2 X_3 + X_1 \bar{X}_2 X_3 + X_1 X_2 \bar{X}_3$$

$m_1, m_3, m_6, m_2, m_5, m_4, m_5$

$$\bar{X}_2 X_3 + X_1 \bar{X}_3 + X_1 \bar{X}_3 + \bar{X}_1 X_2 X_3$$

$$\bar{X}_1 \bar{X}_2 X_3 + X_1 \bar{X}_2 X_3 + X_1 \bar{X}_2 \bar{X}_3 + X_1 X_2 \bar{X}_3 + \bar{X}_1 X_2 X_3 + X_1 X_2 X_3 + \bar{X}_1 X_2 X_3$$

$m_1, m_5, m_4, m_6, m_2, m_6, m_3$

Same

Two functions are equivalent iff their canonical forms are the same


Canonical minterm form

$$f = \bar{X}_1 \bar{X}_2 X_3 + \bar{X}_1 X_2 \bar{X}_3 + \bar{X}_1 X_2 X_3 + X_1 \bar{X}_2 \bar{X}_3 + X_1 \bar{X}_2 X_3 + X_1 X_2 \bar{X}_3$$

$$= m_1 + m_2 + m_3 + m_4 + m_5 + m_6$$


$$= \sum m(1, 2, 3, 4, 5, 6)$$

minimal SOP

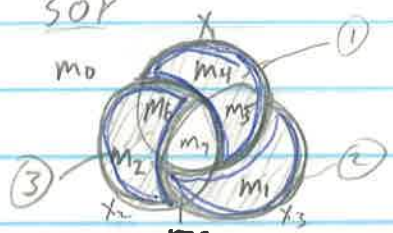

Combining theorem product terms that differ in only one variable can be combined

$$ab^*c + abc = ac$$

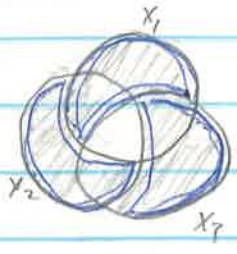

$$f = \bar{X}_1 \bar{X}_2 X_3 + \bar{X}_1 X_2 \bar{X}_3 + X_1 X_2 X_3 + X_1 \bar{X}_2 \bar{X}_3 + X_1 \bar{X}_2 X_3 + X_1 X_2 \bar{X}_3$$


$$= \bar{X}_1 X_3 + X_1 \bar{X}_2 + X_2 \bar{X}_3$$

Alternately

$$\bar{X}_1 \bar{X}_2 X_3 + X_1 X_2 \bar{X}_3 + \bar{X}_1 X_2 X_3 + X_1 \bar{X}_2 \bar{X}_3 + X_1 \bar{X}_2 X_3 + X_1 X_2 \bar{X}_3$$

$$= \bar{X}_1 X_2 + \bar{X}_2 X_3 + X_1 \bar{X}_3$$

cost

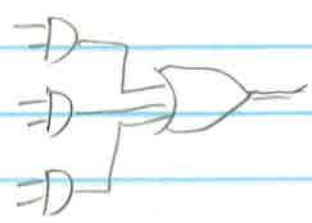

$$\text{cost} = 4 + 9 = 13$$

$$X + X = X$$

#gates + #inputs
4 + 9

another measure = #gates

$$\text{cost of canonical} = 7 + 24 = 31$$


$$\text{cost of original} = 5 + 13 = 18$$

don't count inverters on inputs

$\Sigma m(1,2,3,4,5,6)$
Canonical Maxterm form


$$f = \prod M(0,7)$$
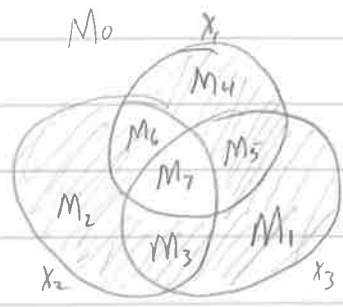
$$(X_1 + X_2 + X_3) (\bar{X}_1 + \bar{X}_2 + \bar{X}_3)$$



$M_0 + M_7$ are not adjacent so they cannot be combined


↑
canonical maxterm form
and minimal POS

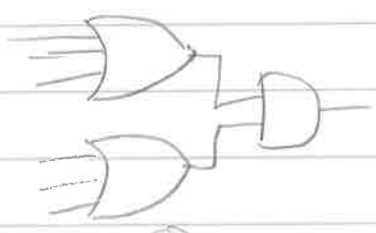




Cost = 3 + 8 = 11 cheaper!

lowest cost circuit

NAND-NAND

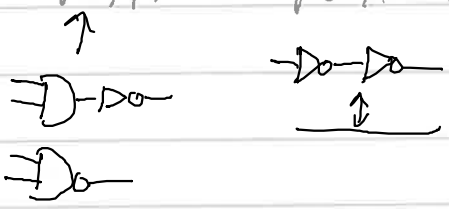




SOP

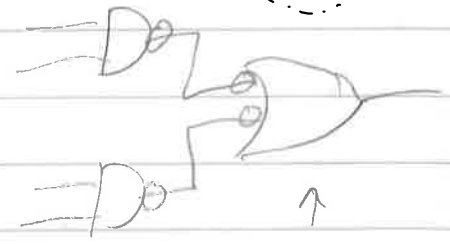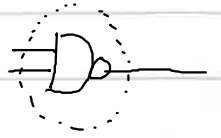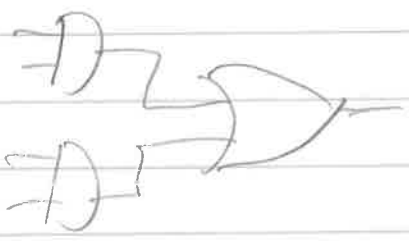

↑
NAND


POS

NOR-NOR

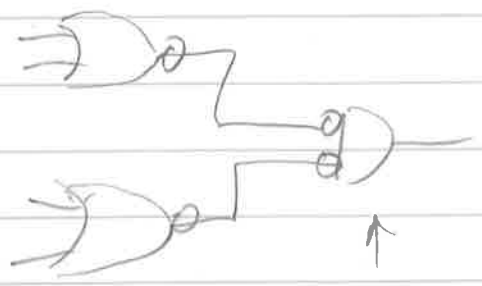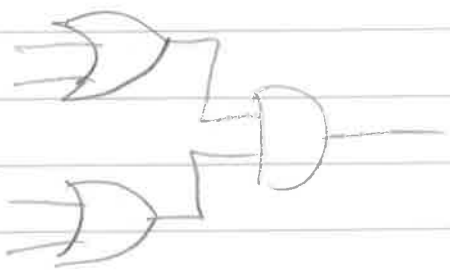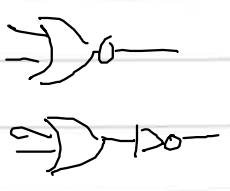

↑
NOR

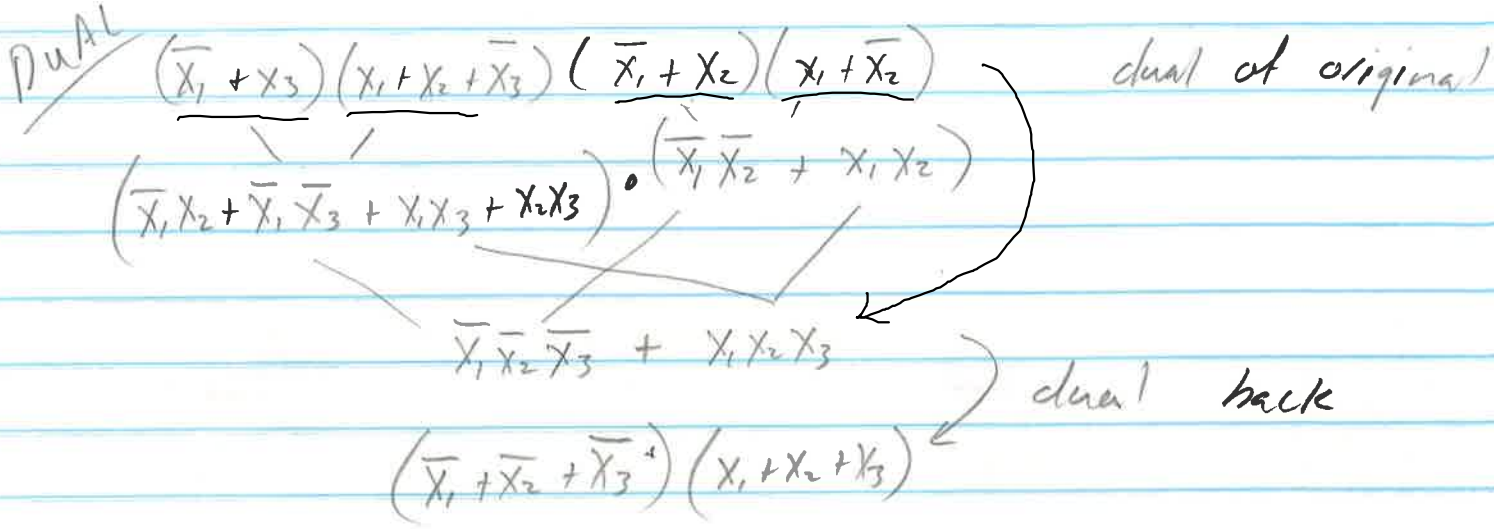Turn SOP into POS (easier to turn POS into SOP so do dual)



without taking dual

