

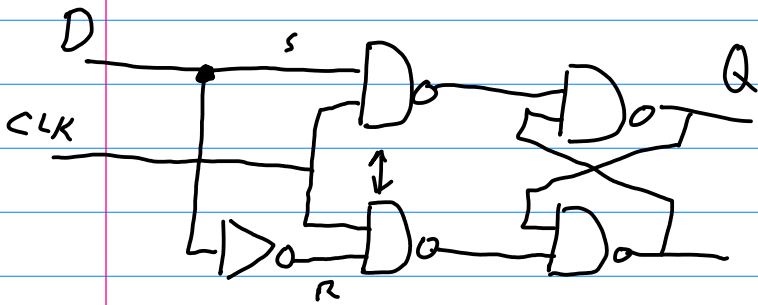





# Gated D-latch

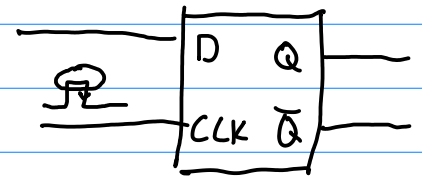


CLK	D	Q
0	X	Q hold
1	0	0
1	1	1

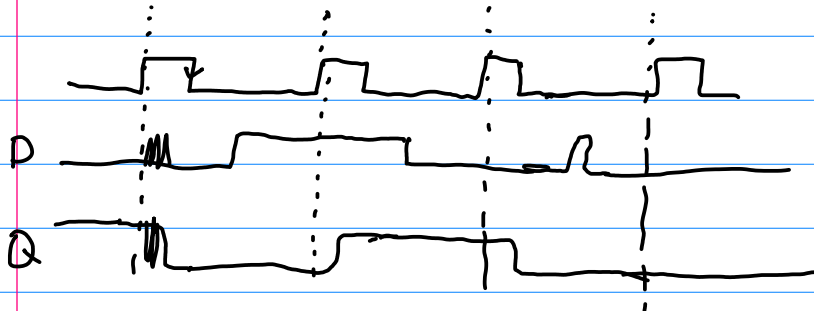

# Master-slave D

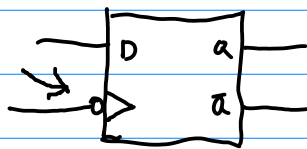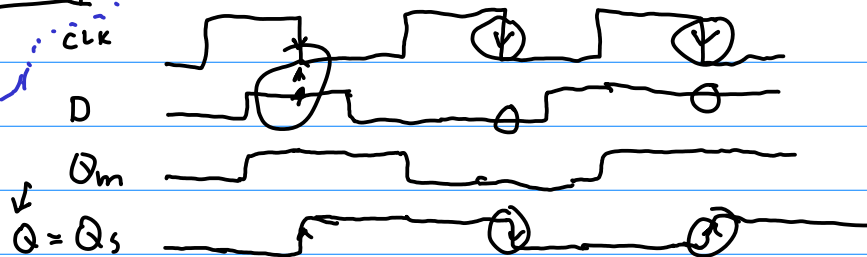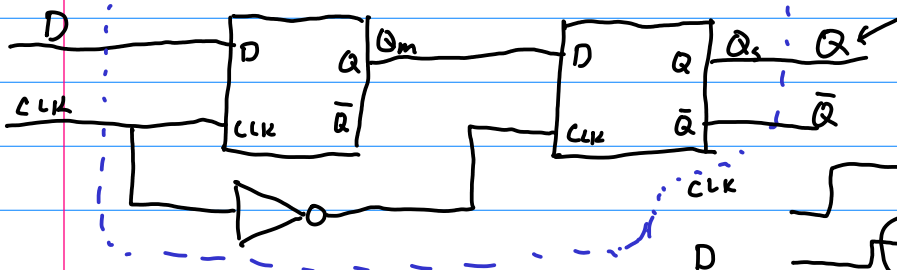

# Edge-Triggered D-ff

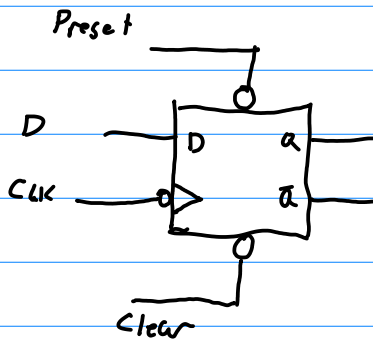

FF goes to 1 on preset  
0 on clear ← has precedence

Asynchronous - happens now  
Synchronous - happens on clock edge

next state

D	Q <sup>+</sup> state
0	0
1	1

Characteristic Equation  
 $Q^+ = D$

T-flip




T	Q <sup>+</sup>	Q	Q̄
0	Q	(hold)	
1	Q̄	(toggle)	

next state (after)  
present state (before)

J	Q <sup>+</sup>	J	K
0	0		
0	1		
1	1		
1	0		

	Q	
	0	1
T	1	0
	Q <sup>+</sup>	

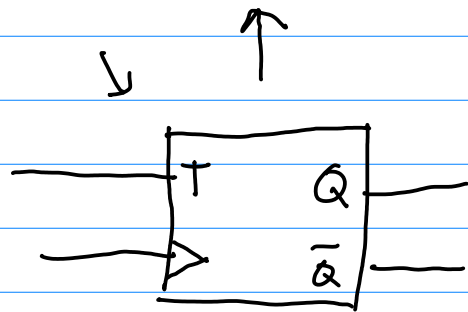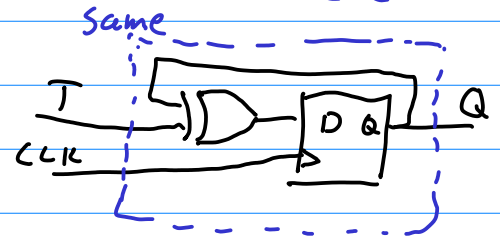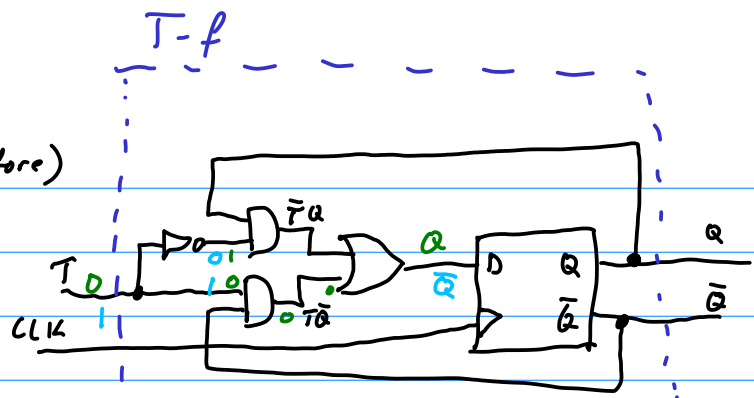Characteristic Equation  
 $Q^+ = \bar{T}Q + T\bar{Q}$   
 D




Jk-flip

J	K	Q <sup>+</sup>
0	0	Q (hold)
0	1	0 (Reset)
1	0	1 (Set)
1	1	Q̄ (Toggle)

Q(t+1)

JR


	00	01	J	
	↓	↓	↓	↓
Q	0	0	1	1
	1	0	0	1
	K		Q <sup>+</sup>	

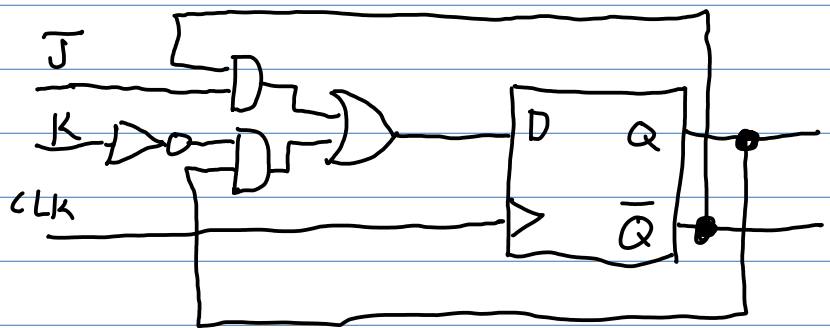

Characteristic Equation

$$Q^+ = \bar{K}Q + J\bar{Q}$$

$$D =$$

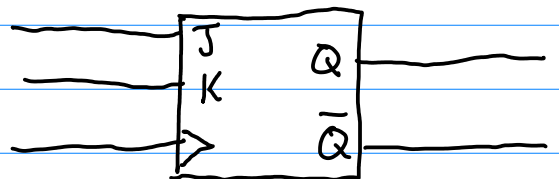

# JK excitation table


J K	$Q^+$
0 0	Q
0 1	0
1 0	1
1 1	$\bar{Q}$

J K Q	$Q^+$
0 0 0	→ 0
0 0 1	→ 1
0 1 0	→ 0
0 1 1	→ 0
1 0 0	→ 1
1 0 1	→ 1
1 1 0	→ 1
1 1 1	→ 0

Q $Q^+$	J K
0 0	0 X
0 1	1 X
1 0	X 1
1 1	X 0

# JK Master-Slave


SR-latches

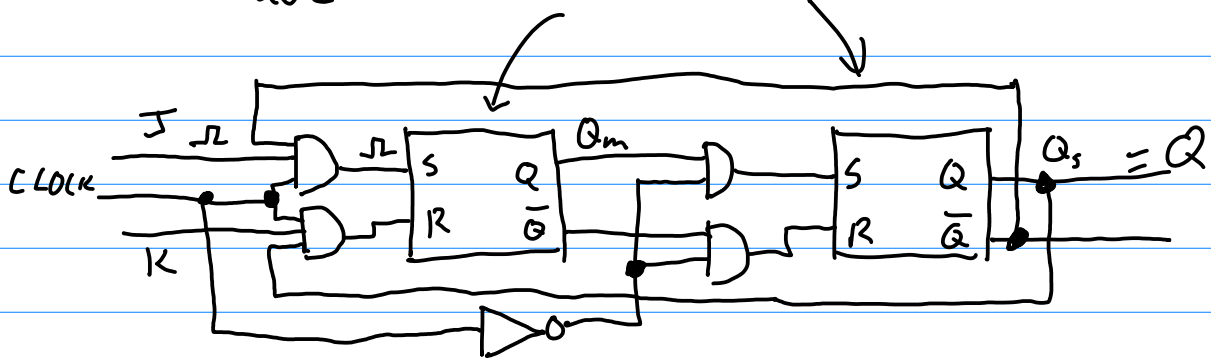

Effectively samples on the falling edge of the clock

Ones Catching:

It is not "true" edge-triggering

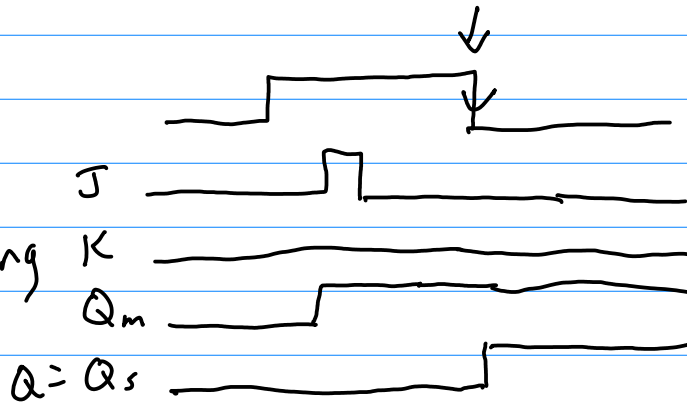


JK from a T - homework

T from a JK

Excitation table

Q	Q <sup>+</sup>	T
0	0	0
0	1	1
1	0	1
1	1	0

J	K	Q	Q <sup>+</sup>	T
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	1

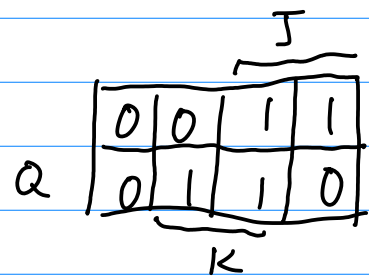

$$T = KQ + J\bar{Q}$$

