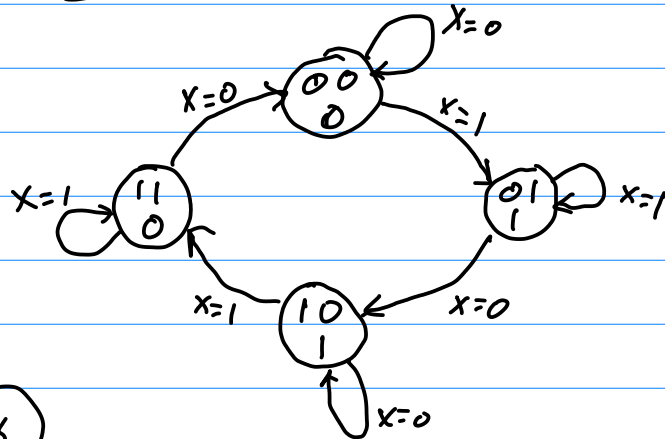




Ex.

Moore - Four states, one input: Each time the input changes, we advance to the next state; Output a 1 iff we are in state 1 or 2.

State graph



P.S. q_1, q_0	N.S.		$Z \leftarrow$
	$X=0$	$X=1$	
00	00	01	0
01	10	01	1
10	10	11	1
11	00	11	0

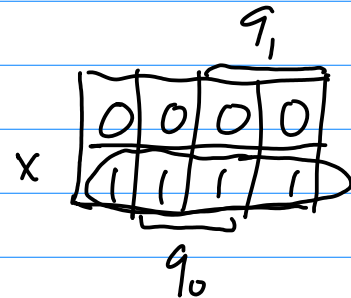
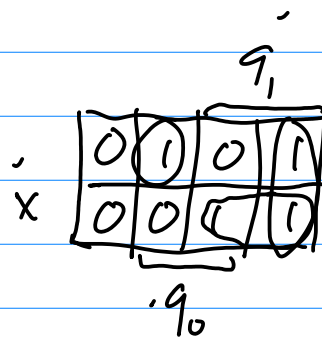


$$D_1 = q_1^+$$

$$D_1 = \dots$$

$$D_0 = q_0^+$$

$$D_0 = X$$

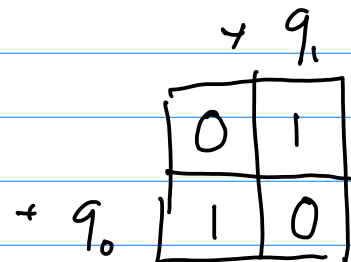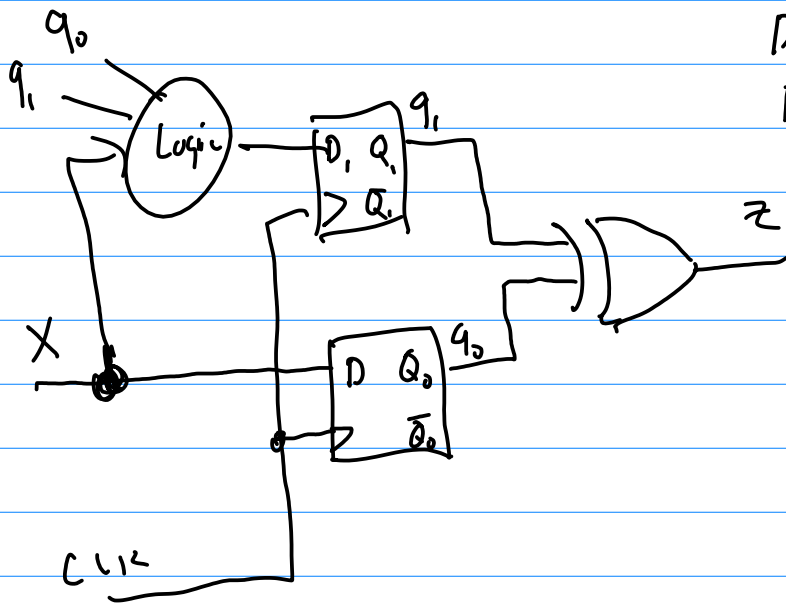

$$Z = q_1 \oplus q_0$$

JK-FF


J	K	Q ⁺
0	0	Q
0	1	0
1	0	1
1	1	\bar{Q}

\Rightarrow

J	K	Q	Q ⁺
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Q	Q ⁺	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

P _S Q ₁ Q ₀	Q ⁺ Q ₀ ⁺ Ns.		Z	X=0		X=1	
	X=0	X=1		J ₁ K ₁	J ₀ K ₀	J ₁ K ₁	J ₀ K ₀
00	00	01	0	0 X	0 X	0 X	1 X
01	10	01	1	1 X	X 1	0 X	X 0
10	10	11	1	X 0	0 X	X 0	1 X
11	00	11	0	X 1	X 1	X 0	X 0

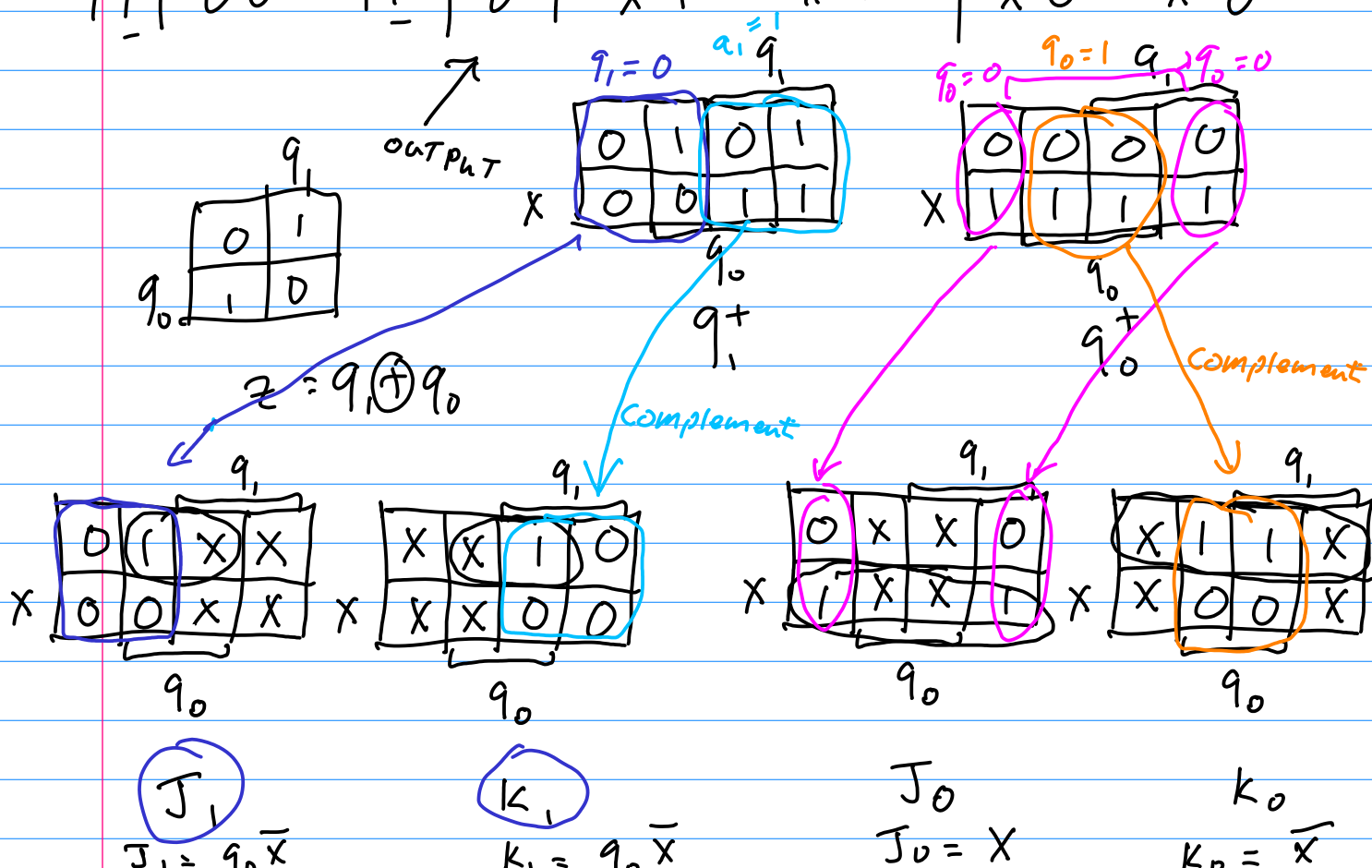

$$J_1 = Q_0 \bar{X}$$

$$K_1 = Q_0 \bar{X}$$

$$J_0 = X$$

$$K_0 = \bar{X}$$

