

Sequential Logic Systems

Digital Logic: The hardware from which computers, watches, cellphones, etc. are built

Moore's Law: the observation that the number of transistors in a dense integrated circuit doubles about every two years. This is an observation that was first made in 1965 and held for decades.

Standard chips: SSI, MSI, LSI, VLSI
Programmable Logic (PLD's, FPGAs, etc.)
Custom Chips, ASIC (Application Specific Integrated Circuits)

Digital vs Analog: Digital has accuracy, repeatability, reliability (consider a watch)


Digital design involves:

System design: how to break an overall system into subsystems

This course → Logic design: how to interconnect building blocks to perform a function
E.g., Gates + flip-flops --> Adder

Circuit Design: how to interconnect specific components
E.g., resistors, transistors to make flip-flops

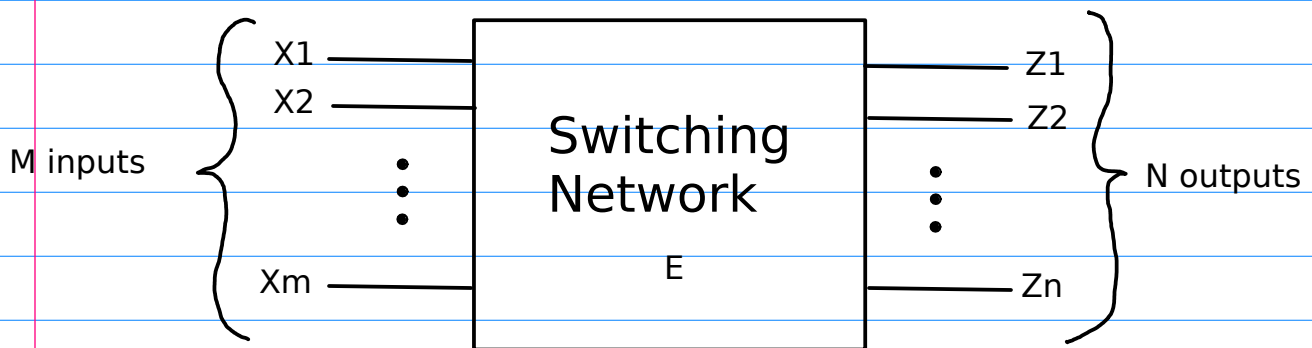Switching Networks (about everything in this course is in this form):



Can be:


Combinatorial - output is a function of the present inputs only (no memory)

Sequential - output is a function of the present and past inputs (requires "memory")

In General a sequential circuit is a combination of a combinational circuit + memory


Example combinational circuits

Truth Table for 3-bit version:

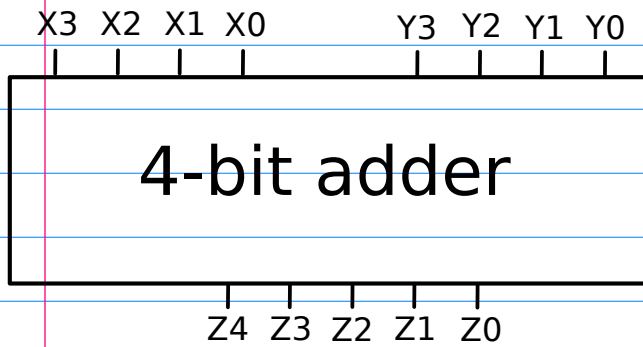


Inputs							Output			
X2	X1	X0	Y2	Y1	Y0	Z3	Z2	Z1	Z0	
0	0	0	0	0	0	0	0	0	0	
0	0	0	0	0	1	0	0	0	1	
0	0	0	0	1	0	0	0	1	0	
0	0	0	0	1	1	0	0	1	1	
			⋮						⋮	
E.g.,										
3+6	→	0	1	1	1	1	0	0	1	
			⋮						⋮	
		1	1	1	1	1	1	1	0	

How about a 32- x 32-bit multiplier?


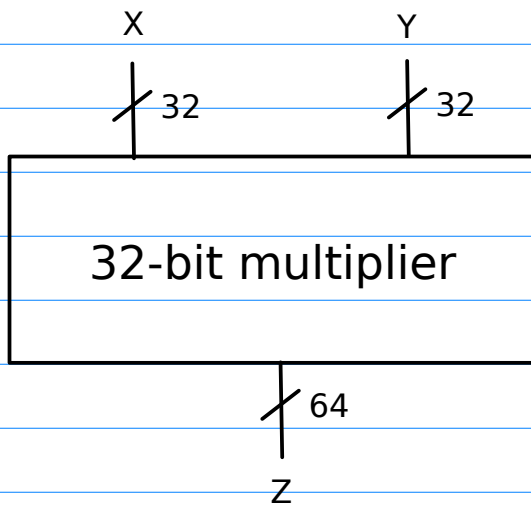


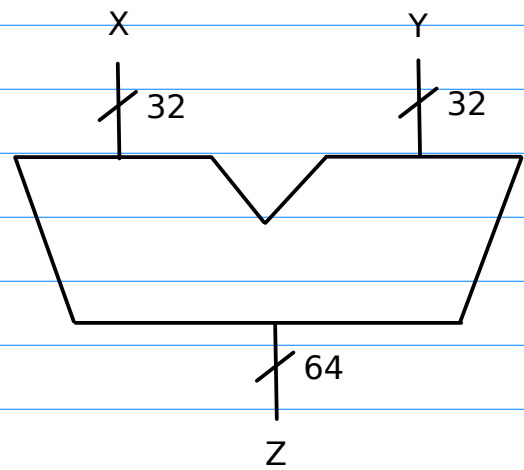Same thing, just an alternate representation



This operation could be "microprogrammed" -- making it sequential inside

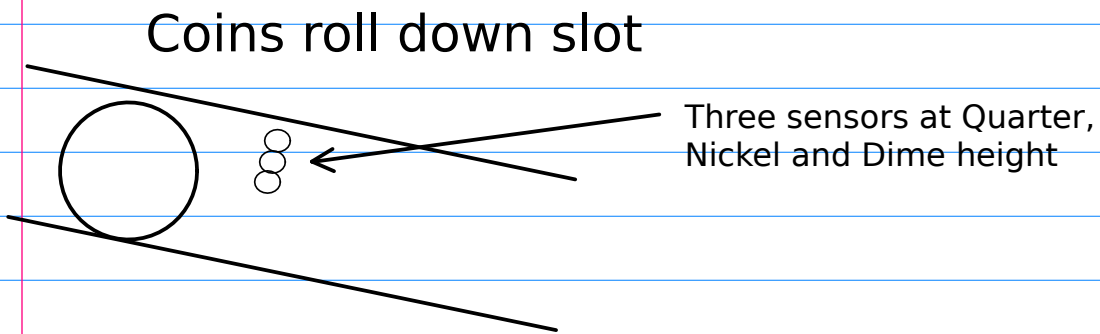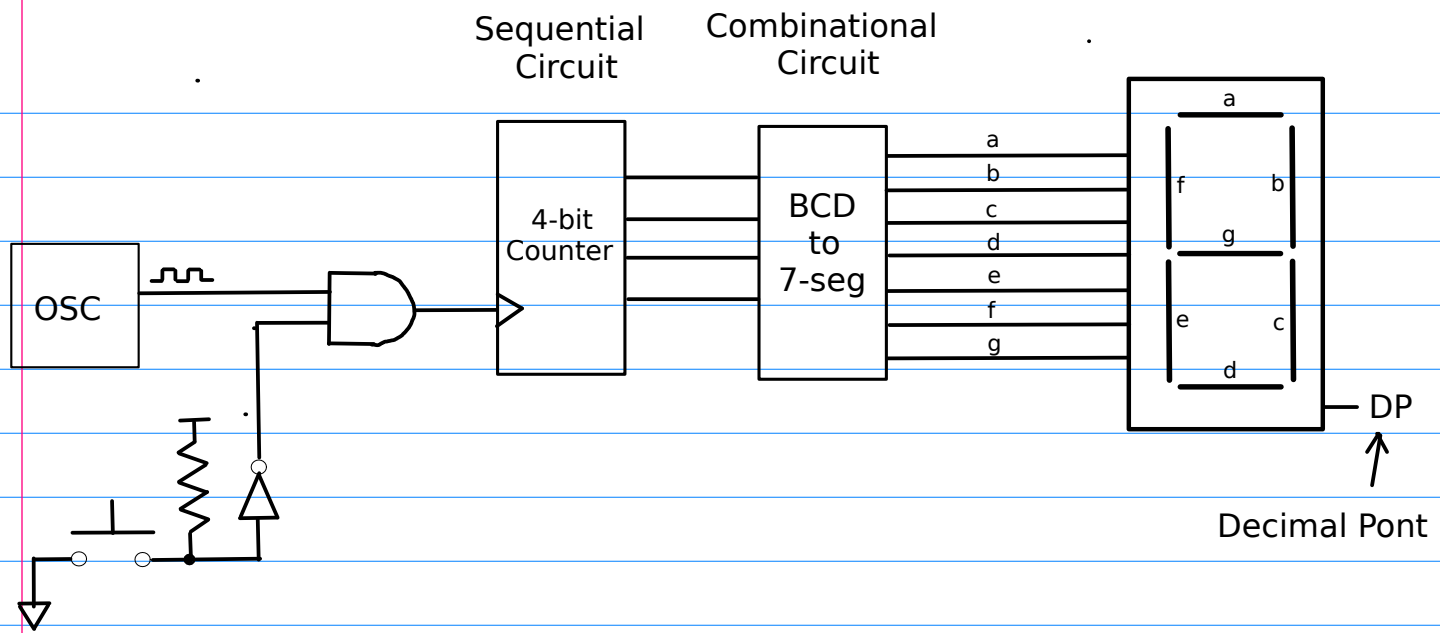It would operate similar to the way humans do multiplication of multiple digits through shifting and adding



Sequential Circuit generates total

