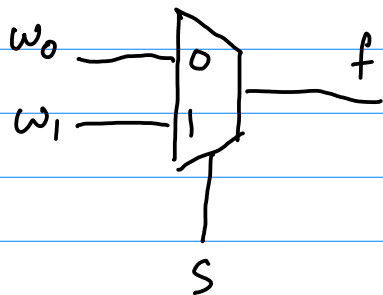



Multiplexers

2:1
mult. plexer




$$f = \bar{S}w_0 + Sw_1$$

4:1
mult. plexer

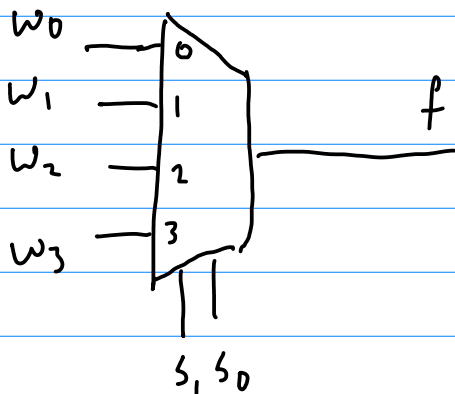
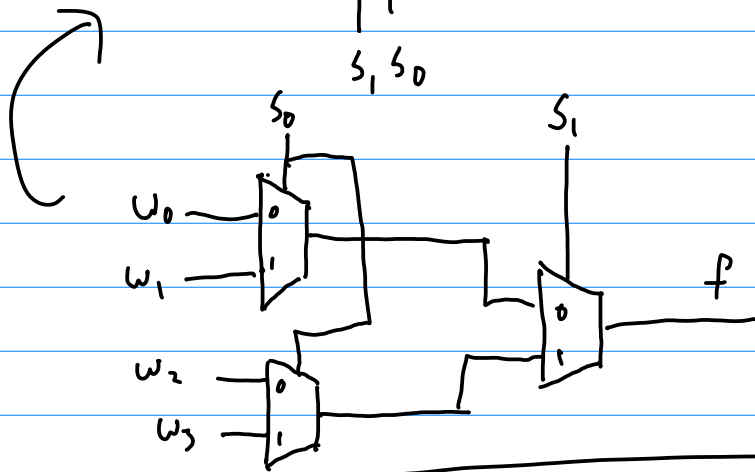
$$f = \bar{S}_1\bar{S}_0w_0 + \bar{S}_1S_0w_1 + S_1\bar{S}_0w_2 + S_1S_0w_3$$



Crosspoint Switch

