

**ECE177: Programming I: From C...**  
**Lab #3 — Setting up the Hardware (Pi Pico and Breadboard)**  
Week of 16 February 2026

## 1 Introduction

In this lab you will set up various pieces of hardware onto a breadboard. You will use this for future labs. The objectives for this lab are to:

1. Wire up the new hardware onto your breadboard
2. Program the Pico with the provided test program to verify your wiring

## 2 Materials

You were previously provided with the following hardware:

- Breadboard with jumper wires
- Raspberry Pi Pico
- micro USB B cable

You will be provided with the following additional hardware:

- Keypad
- LED Bargraph
- TFT LCD
- Speaker
- 18 Resistors, all 510 ohms (green brown brown)
- 8 Pin male to male header

## 3 Assemble the Hardware

- After obtaining the parts start assembling the breadboard. This will be used in future labs.
- Make sure to read all of the directions carefully before getting started!
- Do not power up your board with the USB connector unless you've had the TA verify your wiring first. It is in theory possibly to damage some of the components if you have things wired incorrectly.




### 3.1 Initial Parts Placement and Breadboard Notes




Orient the breadboard such that the red horizontal line (with + sign) is at the top. See Figure 1 for reference.

Note! The breadboards used for in Spring 2026 are strange and new and so they don't match exactly the drawings, and the co-ordinate system is different from previous years. I've done my best to update things, but the row/column numbers in the diagrams aren't going to match exactly what you have. Use the row A...I values from the left side not the right.

Also note the jumper wire colors also changed so they aren't going to match either. Use whatever wire seems to fit properly.


Place the following components.
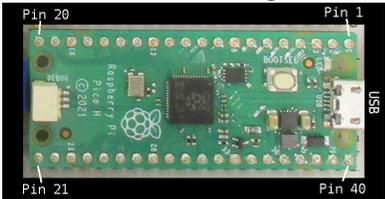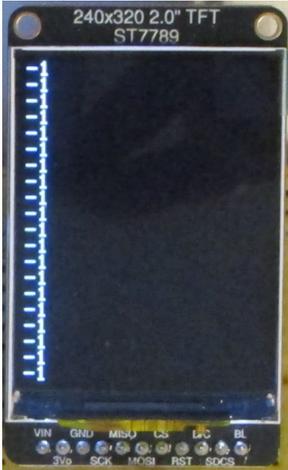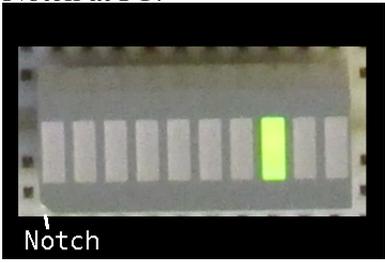
| Part         | Location                       | Notes   |
|--------------|--------------------------------|---|
| RPi Pico     | C42-C61 top and H42-H61 bottom | USB connector on right<br>  |
| TFT Display  | I29-I39                        | The TFT covers the bottom part of the breadboard. Wait to put in until after wiring is complete<br> |
| LED Bargraph | E17-E26 top and F17-F26 bottom | Notch at F17<br>  |
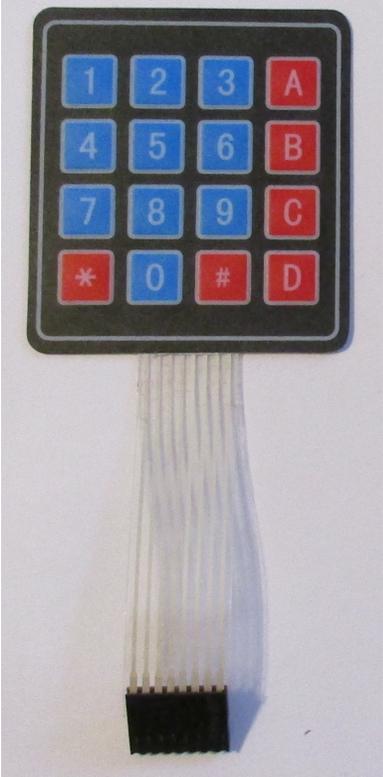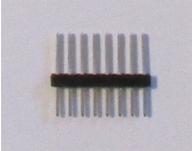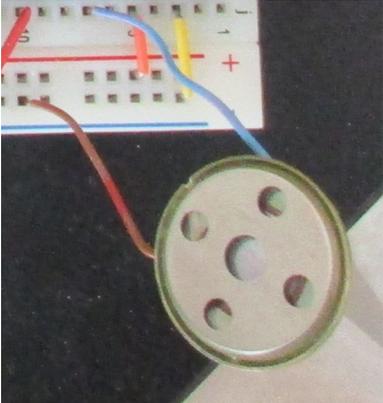
| Part    | Location   | Notes  |
|---------|--|--|
| Keypad  | C4-C11   | <p>Keys should be visible when the keypad is laying down. Use the supplied 8 pin header to connect the keypad to the breadboard</p>   |
| Speaker | <p>Plug in to J55 and to Bottom Blue 55<br/>Note it doesn't matter which wire goes where</p> |    |
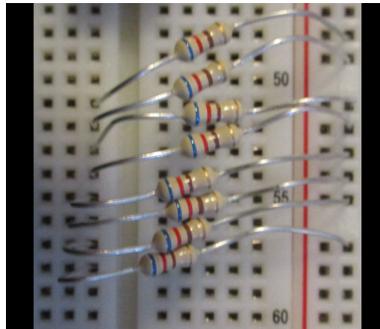
### 3.2 Resistor Placement

You will need to place some resistors on the board. The example here is using 510 Ohm resistors (green brown brown gold) but in the actual lab we might use a slightly different resistance.



Place the resistors in the following locations (note: resistors are symmetrical, meaning it doesn't matter which direction you orient them). Try to avoid shorts caused by their metal legs touching each other.

In the connection tables “Start” is the location to put the first pin (if you look closely there's a marked grid on the breadboards). “End” is where to put the other pin. In this case “Top Blue” means the horizontal blue row at the top of the board. See Figure 1 for reference.

| Start | End            |
|-------|----------------|
| C26   | Top Blue 26    |
| C25   | Top Blue 25    |
| C24   | Top Blue 23    |
| C23   | Top Blue 22    |
| C22   | Top Blue 21    |
| C21   | Top Blue 20    |
| C20   | Top Blue 19    |
| C19   | Top Blue 17    |
| C18   | Top Blue 16    |
| C17   | Top Blue 15    |
| E11   | Bottom Blue 13 |
| E10   | Bottom Blue 12 |
| E9    | Bottom Blue 11 |
| E8    | Bottom Blue 10 |
| E7    | Bottom Blue 8  |
| E6    | Bottom Blue 7  |
| E5    | Bottom Blue 5  |
| E4    | Bottom Blue 4  |

### 3.3 Wiring Phase 1 — Power, Ground, and LED Bargraph

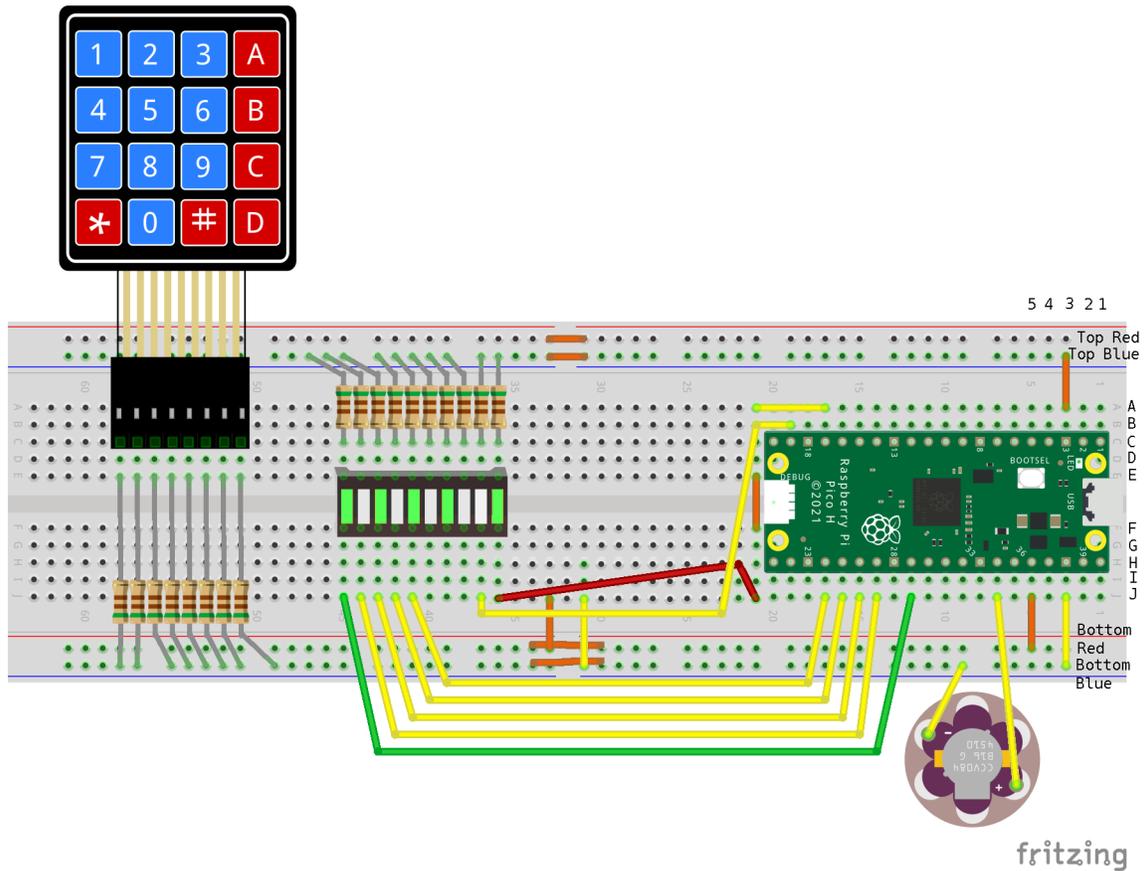


Figure 1: Fritzing diagram showing layout after Wiring Phase 1

Place breadboard jumper wires at the following locations:

| Start         | End            | Wire Color   | Purpose              |
|---------------|----------------|--------------|----------------------|
| Top Red 28    | Top Red 33     | Short Orange | Top Vdd Bridge       |
| Top Blue 28   | Top Blue 33    | Short Orange | Top Ground bridge    |
| Bottom Red 28 | Bottom Red 33  | Short Orange | Bottom Vdd Bridge    |
| Bottom Red 28 | Bottom Blue 33 | Short Orange | Bottom Ground Bridge |
| A59           | Top Blue 59    | Short Orange | Pico Ground          |
| A45           | A41            | Short Yellow | LED10                |
| E41           | F41            | Short Orange | LED10                |
| J59           | Bottom Blue 59 | Short Yellow | Pico Ground          |
| J57           | Bottom Red 57  | Short Orange | Pico 3.3V Out        |
| J29           | Bottom Red 29  | Short Orange | TFT power            |
| J31           | Bottom Red 31  | Short Yellow | TFT ground           |
| J50           | J17            | Green        | LED 1                |
| J44           | J18            | Yellow       | LED 2                |
| J47           | J19            | Yellow       | LED 3                |
| J46           | J20            | Yellow       | LED 4                |
| J45           | J21            | Yellow       | LED 5                |
| J41           | J26            | Red          | LED 10               |
| B43           | J25            | Yellow       | LED 9                |

### 3.4 Wiring Phase 2 — Complete LED Bargraph

Remove the TFT display and add the following wires

| Start | End | Wire Color | Purpose |
|-------|-----|------------|---------|
| B42   | J24 | Yellow     | LED8    |
| J42   | J23 | Orange     | LED7    |
| J43   | J22 | Orange     | LED8    |

Leave the TFT display unplugged for now.

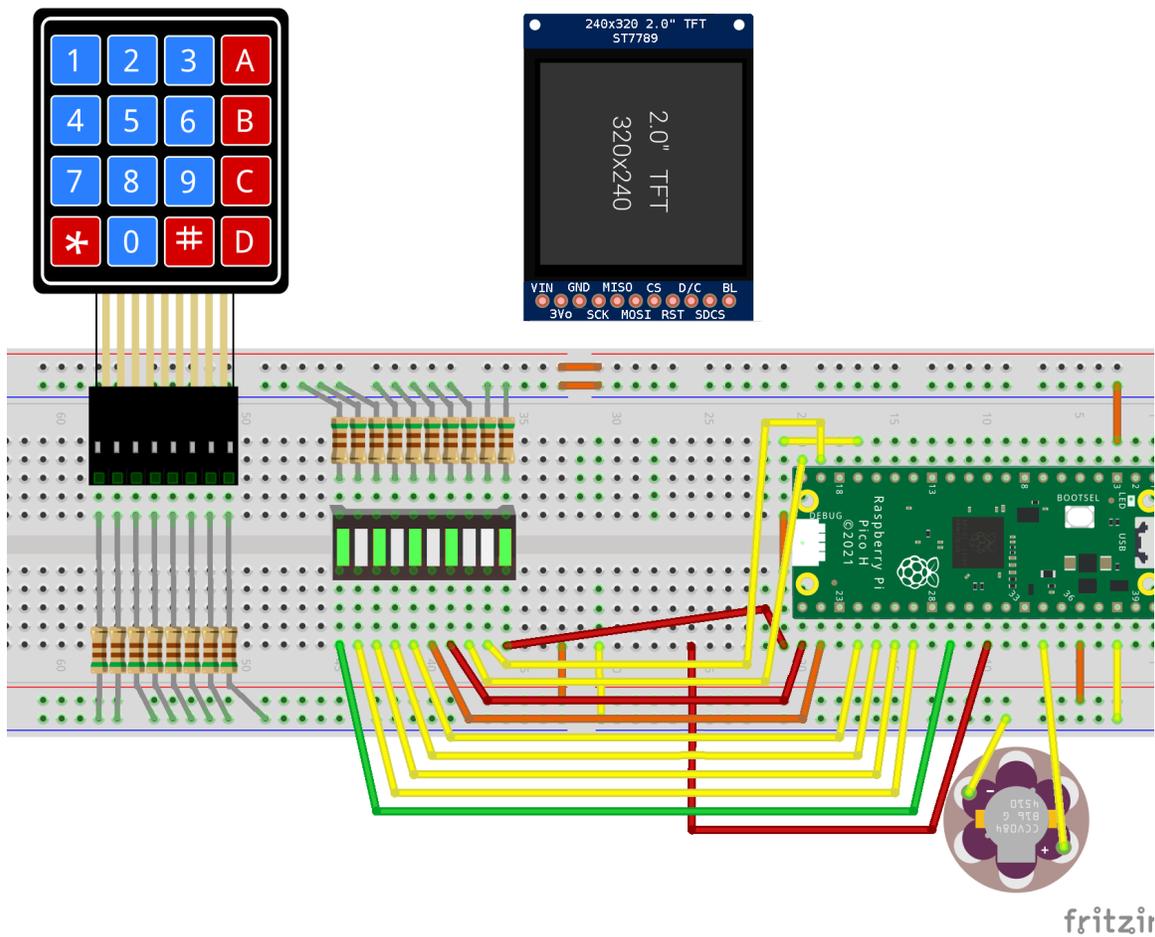


Figure 2: Fritzing diagram showing layout after Wiring Phase 2





### 3.7 Wiring Phase 5 — Final Assembly

Plug the TFT display back into the breadboard at I22-I33. Plug the keypad back into C51-C58.

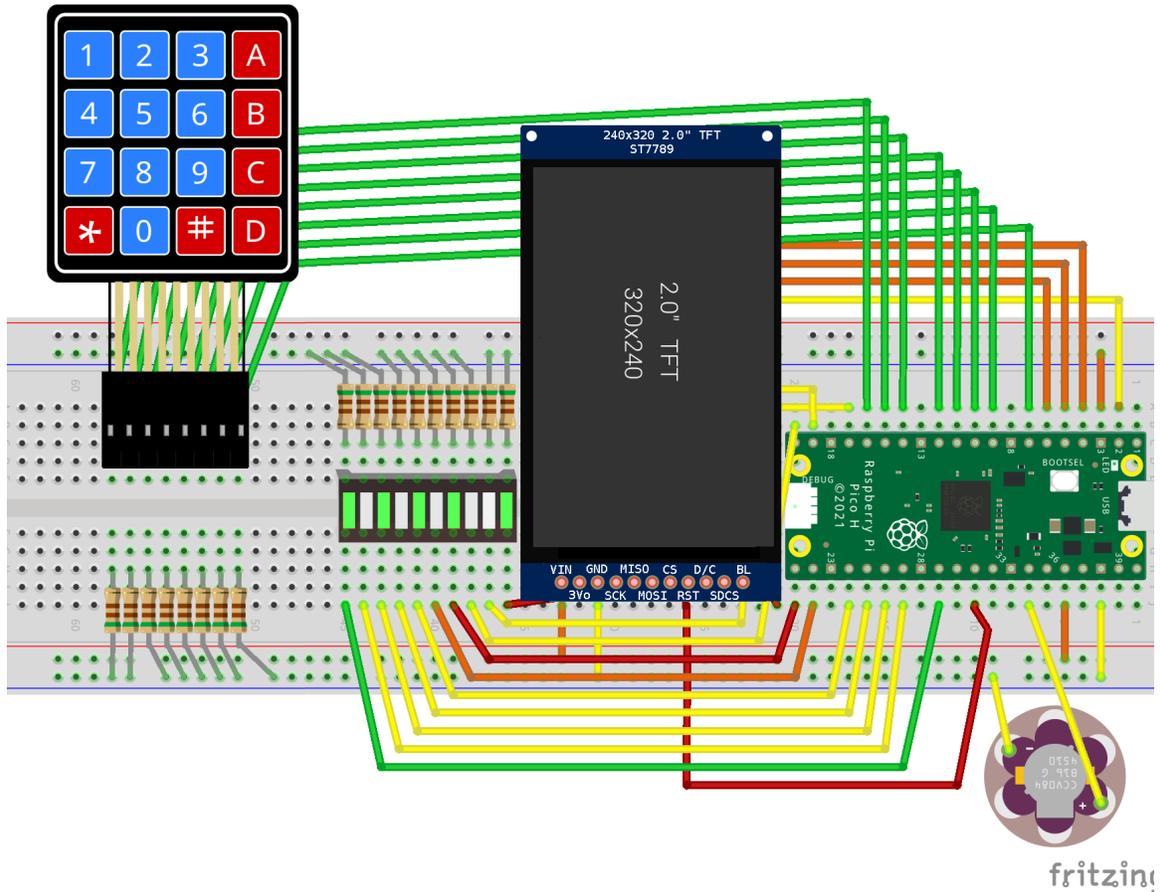


Figure 5: Fritzing diagram showing final layout

## 4 Test The Hardware

Before proceeding to the next step, have a TA check the wiring using the following criteria

| Points | Accuracy             |
|--------|----------------------|
| 4      | No errors            |
| 3      | One error            |
| 2      | Two errors           |
| 1      | More than two errors |

Please fix any wiring issues before continuing.

## 4.1 Installing the Test Code

1. Download the test code:  
[https://web.eece.maine.edu/~vweaver/classes/ece177/labs/lab03\\_code.zip](https://web.eece.maine.edu/~vweaver/classes/ece177/labs/lab03_code.zip)
2. Uncompress this and you should get the file `lab03.uf2` which is a pre-compiled test program we will load onto the Pi Pico
3. Plug in the Raspberry Pi Pico into your laptop while holding down the white “BOOTSEL” button
4. If you do this, your Pi Pico should appear as an external drive on your computer. (On windows this is often the D: drive)
5. In this mode you can program the pico by dragging a `.uf2` file into this drive
6. Program the Raspberry Pi Pico by copying the `lab03.uf2` file into this drive (On Windows you can do this by dragging `lab03.uf2` into the drive folder)

## 4.2 Running the Test Code

If all went well the following should be happening:

- The Raspberry Pi Pico should now have a green blinking LED.
- The LED bar graph should be sequentially blinking and all bars should be able to light up.
- The LCD display should be displaying “-1”.

**If this does not happen, and especially if any part gets hot, immediately unplug the USB cable and re-check your wiring!**

### 4.3 Test the Keypad

Verify the functionality of the keypad by pressing each button and comparing the output with the following table.

| Input | Output              |
|-------|---------------------|
| 0     | 2 0                 |
| 1     | 15 1                |
| 2     | 14 2                |
| 3     | 13 3                |
| 4     | 11 4                |
| 5     | 10 5                |
| 6     | 9 6                 |
| 7     | 7 7                 |
| 8     | 6 8                 |
| 9     | 5 9                 |
| A     | 12 12               |
| B     | 8 13, Start speaker |
| C     | 4 14, Stop speaker  |
| D     | 0 15                |
| *     | 3 10                |
| #     | 1 11                |

## 5 Some Last Notes

- You will need this assembled board for all future labs
- It might be useful to have some sort of case to protect it so the wires don't come loose
- Please do not bend severely or crease the keypad ribbon cable as it can break

## 6 Grading/Checkoff

1. Please upload a picture of your completed board running the test code to brightspace.
2. TAs will check the wiring of your breadboard and then ask you to demonstrate the working code on your hardware. The TAs will enter grades after verifying your hardware is working with the lab03 code.
3. TAs: Enter grades only after verifying full functionality of all LEDs, keypad buttons, TFT display, and speaker sound.

## 7 Troubleshooting

Here are just some notes on what to check if your wiring looks good but various parts aren't working after programming.

- **Pi Pico won't program**
  - Try pulling the Pi out and programming it not in the breadboard. If that works there's something wrong with your wiring
  - The big thing to check is if the power and ground lines are connected properly. The most common mistake is having the wire in the lower right that is supposed to be connected to ground going to the wrong pin
- **Pi powers up (green LED blinks) but LCD Display does not Print -1**
  - This means some of the wires going to the LCD are hooked up wrong. Take it off the board and make sure the wires are going to the right holes, it's easy to be off-by-one here
- **Pi powers up, but the LED bargraph does nothing**
  - Be sure the top ground plane (horizontal blue line) is jumpered across so that the resistors are getting proper ground
  - Be sure the bargraph is installed in the right orientation (if installed backwards an LED will not light up)
- **Some of the keypad rows/columns are not working**
  - Try running with a "known good" keypad. If a good one works, it means yours might be broken (this happens sometimes)
  - If the known good one fails the same way then double check your wiring