

ECE 214 – Electrical Circuits Lab

Lecture 5

Vince Weaver

`http://www.eece.maine.edu/~vweaver`

`vincent.weaver@maine.edu`

17 February 2015

Announcements

- Midterm next week (Tuesday the 24th)
- Lab notebooks due (Thursday the 26th by 5pm)
- No lab next week! (Unless you are Monday lab).
Labs will resume with Lab#6 after spring break.
- No Monday lab immediately after break.



Microcap

- Postlab. Op-amp problems?
- Try using the “Generic” op-amp which you can find on the side bar.
- Make sure when you create a 1M resistor use 1meg or 1000k. 1m means 1 mili-ohm.



Notes from Previous Labs


- Why might you get a gain of -10 rather than -4.7 on Inverting Op-amp?
Know your color codes! Resistors soldered in wrong place on board.
- Integrate: sine/cosine, square/triangle, triangle/parabolas (not sine), sawtooth/bumpytops
- derivative: sine/cosine, square/impulse, triangle/square (ringing)



- Analog Computers



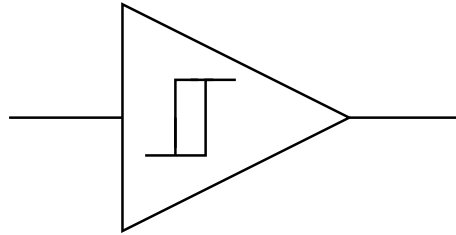
Lab #5 – Schmitt Trigger and Oscillator Circuit



- Invented by Otto H. Schmitt in 1934 as a grad student.
- What are they good for?
- De-bouncing switches?



PreLab

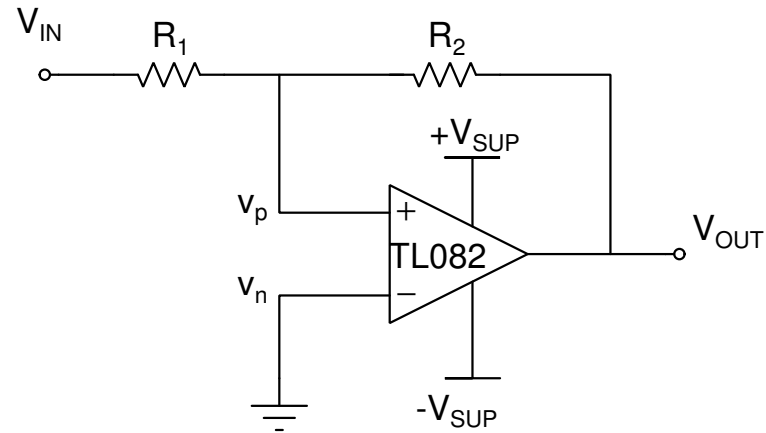


- Positive Feedback (Input to +), running in saturation
- If $v_p > v_n$, $V_{OUT} = V_{SUP}$
- If $v_p < v_n$, $V_{OUT} = -V_{SUP}$




- Superposition principle: calculate each node, setting other V source to 0. Then add.

- $V_n = 0, V_p = \frac{R_2}{R_1+R_2}V_{IN} + \frac{R_1}{R_1+R_2}V_{SUP}$

- $V_{IN} = \pm \frac{R_1}{R_2}V_{SUP}$

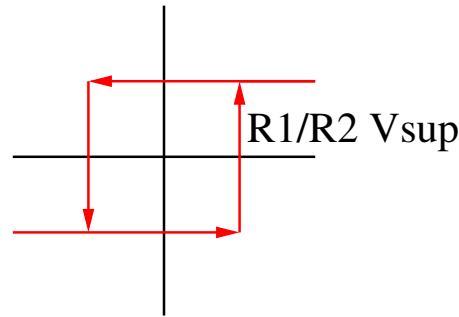

Using a Single Rail

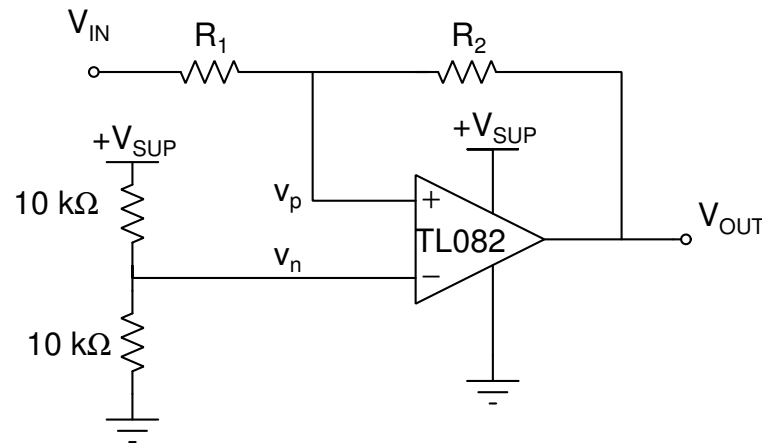


- Calculate so levels separated more than 3.5V but less than 4.5V When supplies 10V and GND
- Use the equation before, then just shift up by 5V at the end.



- Make sure current through resistor less than 10mA
- CAUTION! BUILDING THE CIRCUIT
Connect V_+ to 10V, GND and V_- together to GND.
Do not hook up -10V anywhere!
- The parts are not all going to be available on the board, so use a breadboard (on the TI board or your own)
- Your calculated values might not give close enough results. Real-world op-amps are not ideal!



Oscillator

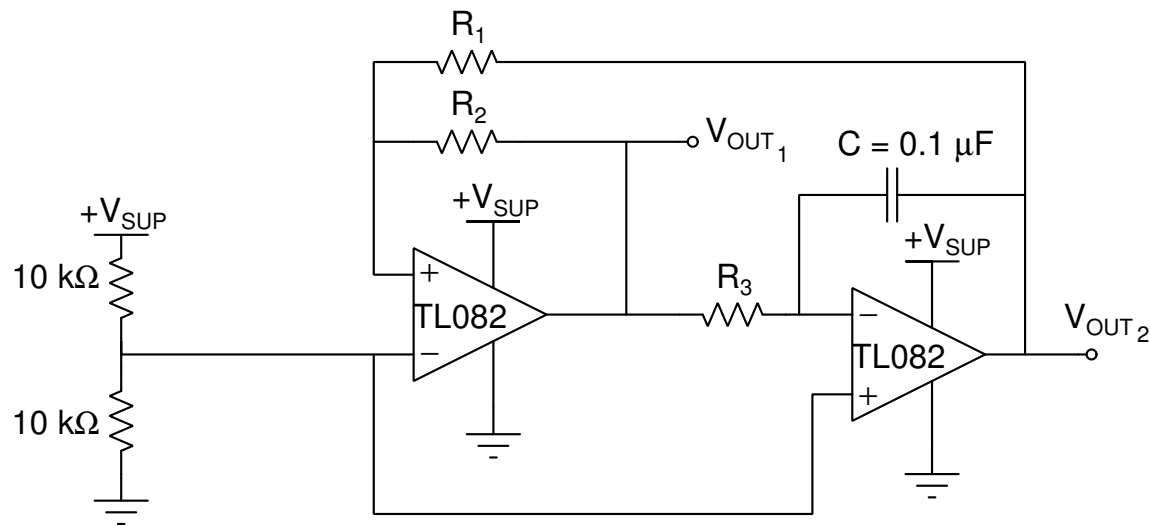


- A Schmitt trigger hooked to an inverting integrator with feedback.



- It has just flipped, to flip back has to go back down by $2*(R_1/R_2)$
- $I_C = \frac{V_S}{R_3}$
- $\Delta t = \frac{C\Delta V}{I_{R3}}$
- Substitute; $\Delta t = 2\frac{R_1}{R_2}V_s\left(\frac{1}{\frac{V_s}{R_3}}\right) = \frac{2R_1R_3}{R_2}C$
- $T = 2\Delta t = \frac{4R_1R_3}{R_2}C$
- $f = \frac{1}{T} = \frac{R_2}{4R_1R_3C}$



Reducing even Harmonics

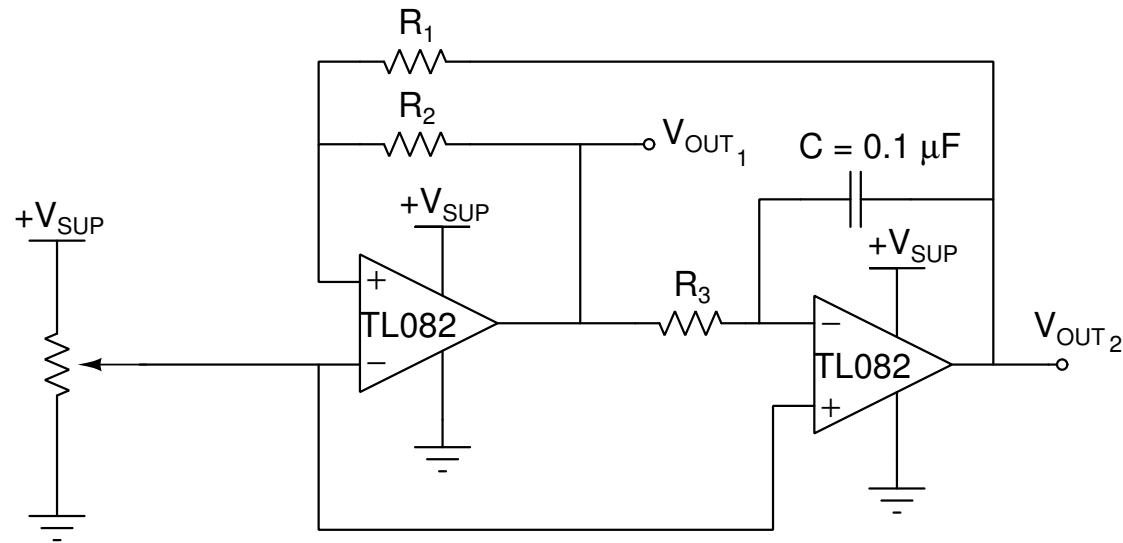

- View the square wave in FFT mode.
- Are there large even harmonics? If so then you can



reduce them by adjusting the DC offset.

- Put a variable resistor into the input and adjust the voltage offset until the even harmonics are minimized.



Question

- If circuit starts out exactly in balance, how does oscillation start?
- May be a problem if you try to simulate with microcap.
- In real world enough random noise to kick off (unstable equilibrium).



Postlab

- None this week.




Midterm

- During lecture next week
- Open lab-book. Can use calculator. No laptops.
- Know how to read an oscilloscope display
This includes voltages, times, Lissajous, and Fourier screens.
- Know how to set up a function generator.
- Be able to quickly find and answer questions on the pre,



lab, and post from your lab book.

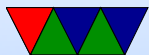

Lab-notebooks

- Turn in by 5pm Thursday the 26th.

