

ECE 214 – Electrical Circuits Lab

Lecture 6

Vince Weaver

`http://www.eece.maine.edu/~vweaver`

`vincent.weaver@maine.edu`

17 March 2015

Announcements

- Lab re-starts this week!
- Remember you can change up lab partners



Midterm Review

1. Test Equipment

(a) Oscilloscope plot. What does the "1 1.0V" mean?

- i. V_{pp} Signal 1 = Peak to Peak = 8V
- ii. V_{pp} Signal 2 = 4V
- iii. Period = 2ms. Frequency = $\frac{1}{T} = 500\text{Hz}$
- iv. Phase shift = $f \cdot dt \cdot 360$ or just note is $360/10$ blocks
= 36 degrees

(b) Lissajous.

$$\sin^{-1}\left(\frac{1.4142}{2}\right)$$



Watch your sig figs, and watch your rounding!

2. RC Circuits

(a) i. high pass filter

ii. 3rd order

iii. $\frac{1}{2\pi RC} = 750.7\text{Hz}$

iv. 60dB/decade

(b) Bode plot. Cutoff at 751Hz, drop 60 dB/decade, high pass.

3. OpAmp



- (a) Gain is $-\frac{R_2}{R_1} = -2$
- (b) Plot is twice as big, inverted.

4. Schmitt Trigger

- (a) Hysteresis plot. $-V_{sup}$ to V_{sup} and $-\frac{R_1}{R_2}$ to $\frac{R_1}{R_2}$.
Did not want square/triangle wave output.

5. Schmitt Trigger Oscillator

- (a) $V_{out1} = \text{Square}$
- (b) $V_{out2} = \text{Triangle}$
- (c) $f = \frac{R_2}{4R_1R_3C}$. Solve, $R_3 = 500\Omega$



6. Space ship question.




Lab Notebooks


- Overall good
- Follow directions. Plots, semi-log. Label axes.
- Micro-cap. Know it's a pain. For the integrator plots, main issue was getting $\pm 5V$, not starting at zero. Calculus. Op-amp issues.




Lab #6 – DC – DC Converter

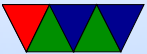


Diodes

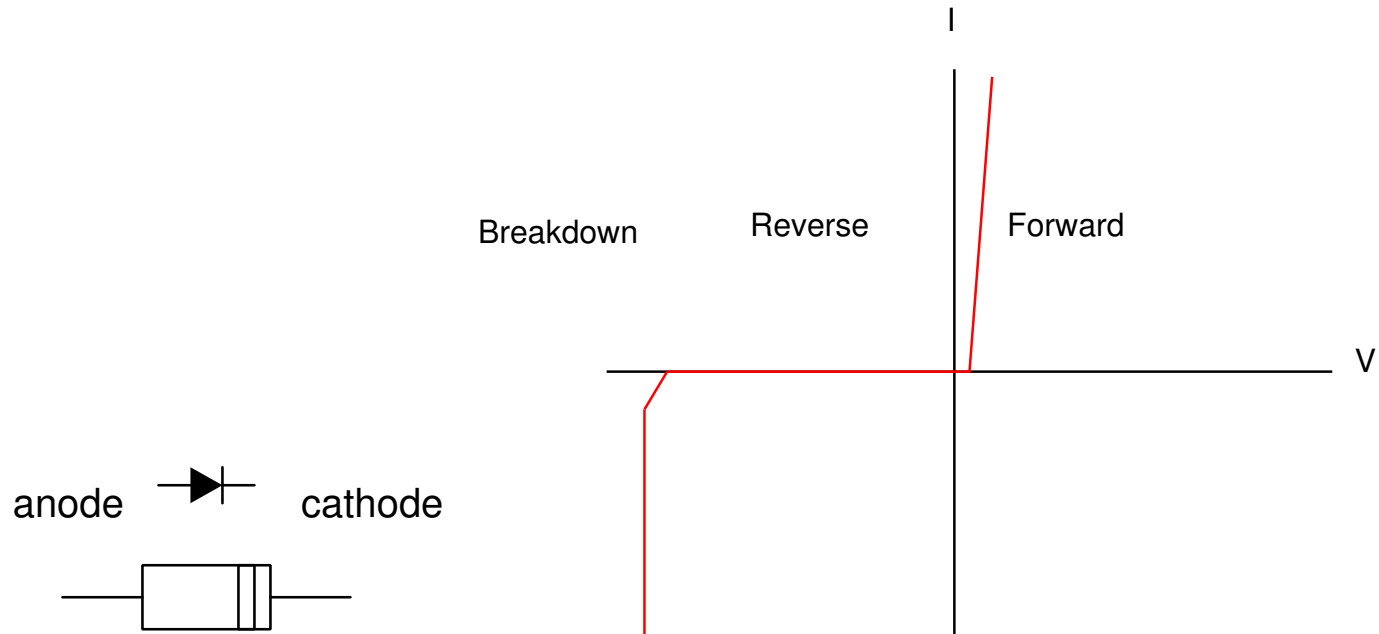

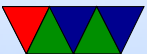- Many kinds: signal, zener, photo, schottky, (my favorite) LED.




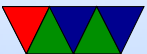- Block current going one way (ideal).
Real world more complicated; too much reverse voltage and will eventually breakdown. Also have a forward voltage drop (typically around 0.6V for Si diodes).
- Zener diodes have breakdown voltage of values like 5V, can be used for simple power supplies.




AC/DC conversion

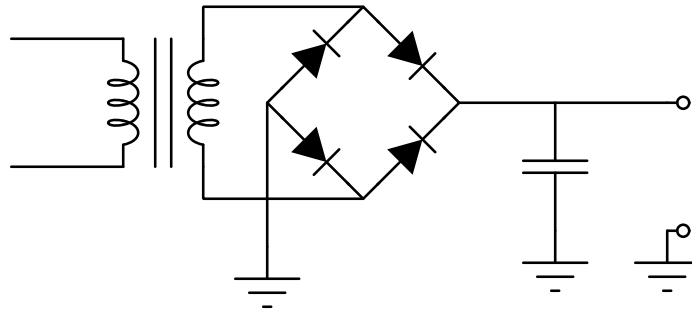- Motor feeding into a generator?
- Huge transformer with differing coils
- Bridge rectifier




Villard Doubler

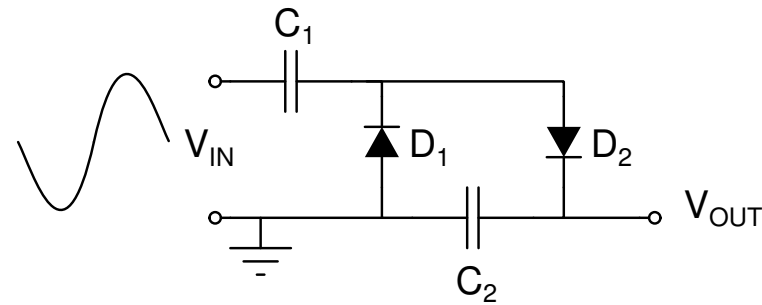

- Technically the Villard Circuit only has one diode and one capacitor and doesn't behave well.
- We'll actually be building a Greinacher circuit. Also called a Cockroft-Walton multiplier




Negative Half

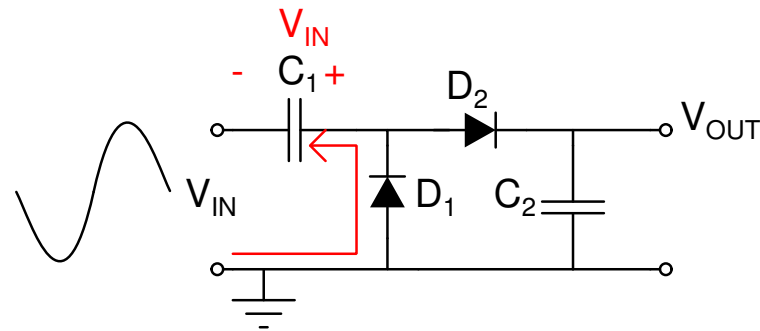


- D_1 Turns on, Charges C_1 to V_{IN}



Positive Half

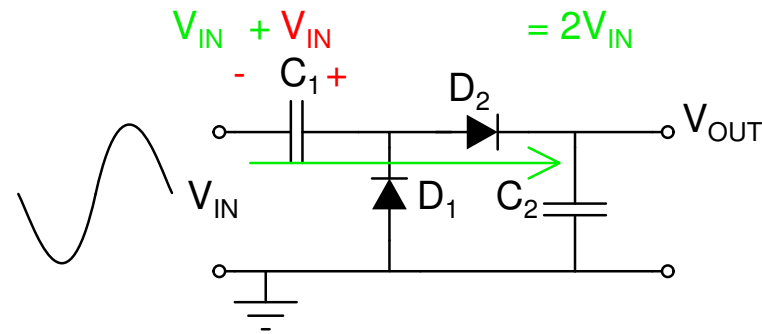


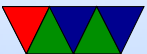- D_1 Turns off, D_2 Turns on, Output is $C_1 + V_{in}$.
- C_2 charges to $2 * V_{in}$



Ripple

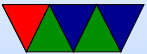- Formula: $V_{ripple} = \frac{I_{load}}{(2fC)} * n * (n + 1)$
- I = current load, f = frequency, C = capacitance, n = number of stages (1 in our case)



Drop

- Formula: $V_{drop} = \frac{I_{load}}{(6fC)} * (4n^3 + 3n^2 - n)$
- I = current load, f = frequency, C = capacitance, n = number of stages (1 in our case)
- Also worry about voltage drop in diodes (0.6V?)




Multiple Stages

- Can multiply out an arbitrary number
- Ripple will increase. can be mitigated somewhat by increasing capacitor values.
- What tolerances for cap/diode?
- USB destroyer in the news

<http://hackaday.com/2015/03/11/killer-usb-drive-is-designed-to-fry-laptops/>



Circuit to Build

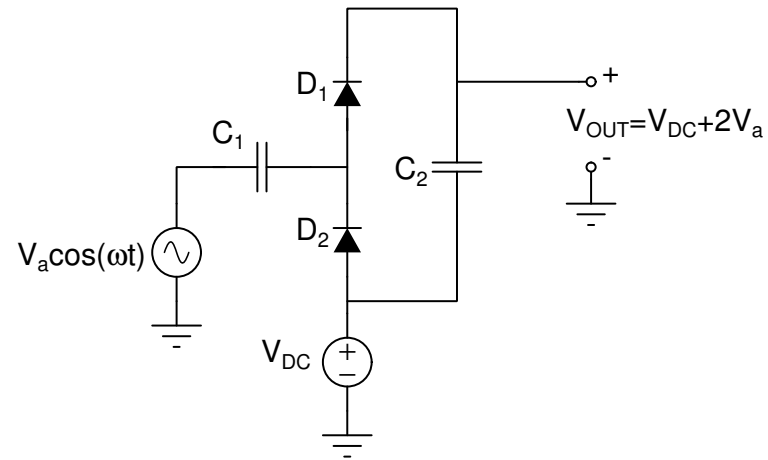

- Want to input 10V DC, get more than 15V DC out.
- Can you double DC alone?
No, you need some sort of AC component.




PreLab

- Design it.
- Run it through micro-cap.
- Use 1N4001 in microcap. Also pick a cap value from 10nF to 100nF.
- Remember to include oscilloscope output resistance, etc.



Lab

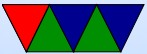- Build it.
- The diodes available in lab are 1N4004. See data sheet for difference (hint, breakdown voltage)



Postlab

- Compare.
- Write-up

