
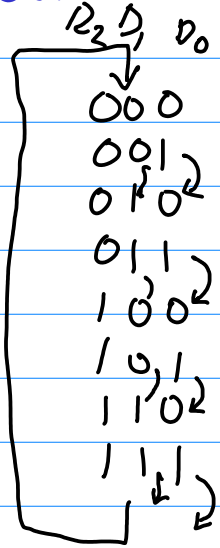


Counters:


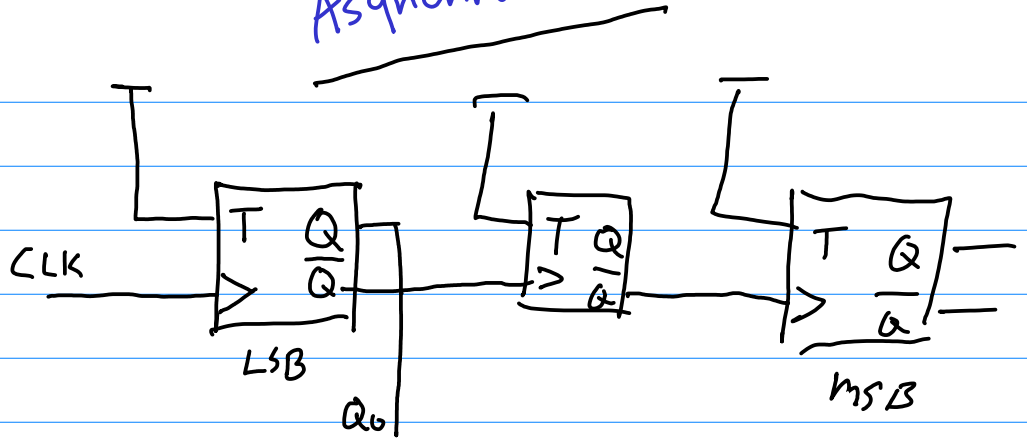


Asynchronous



Note Ripple!

Count Down

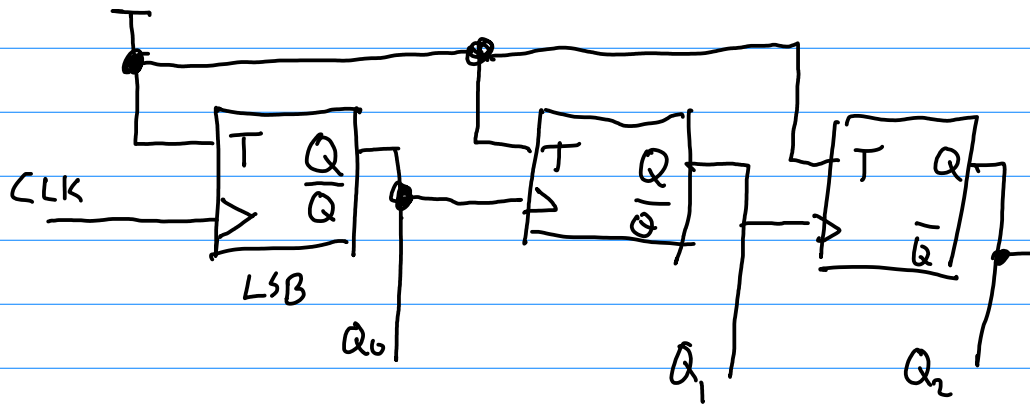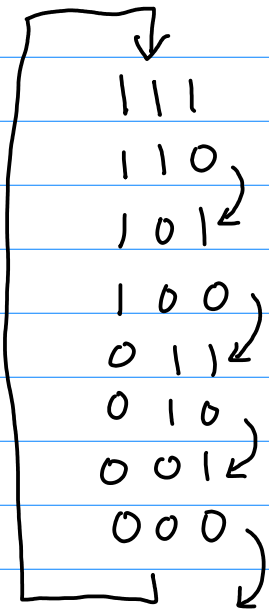


Asynchronous: Bits don't all change at the same time


Synchronous — same clock goes to all flip-flops

Q_3, Q_2, Q_1, Q_0

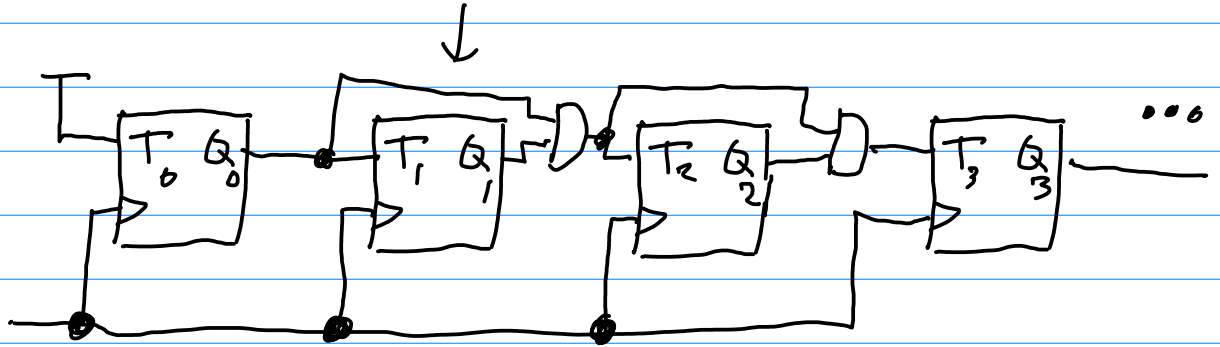
- 0000
- 0001
- 0010
- 0011
- 0100
- 0101
- 0110
- 0111
- 1000
- 1001
- 1010
- 1011
- 1100
- 1101
- 1110
- 1111




Enable & Clear

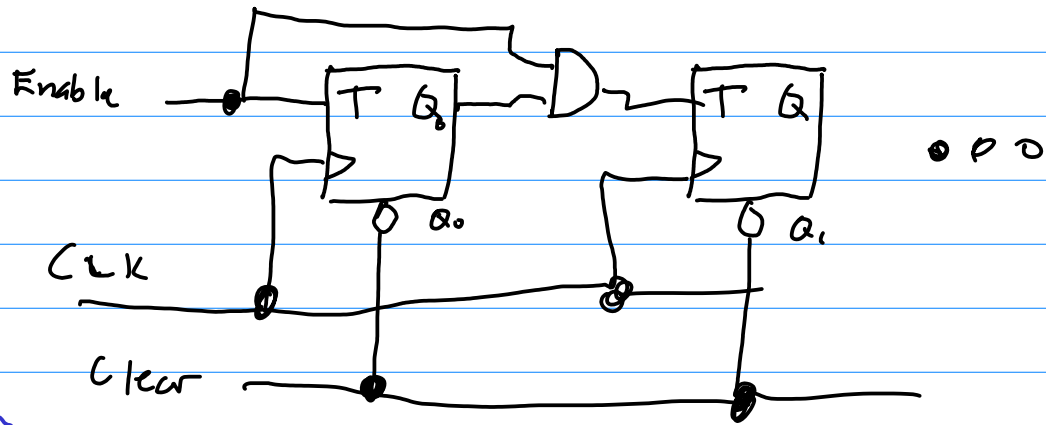

T-fl

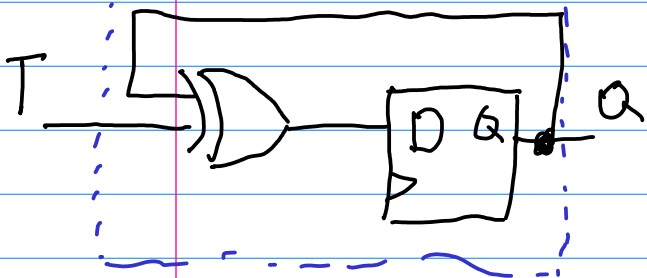


↑

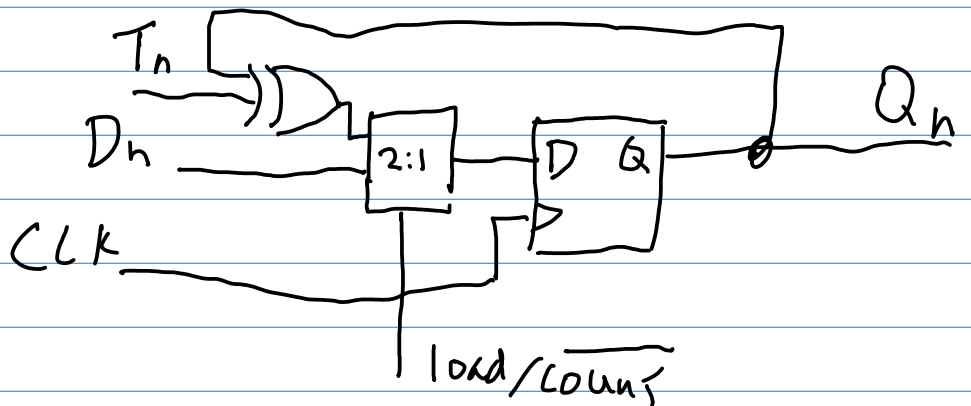


Modulo-n counter


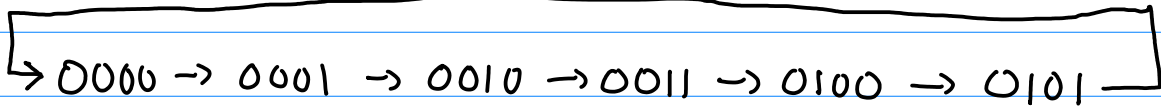
Note BCD counter would go to 9 and then reset




Asynchronous

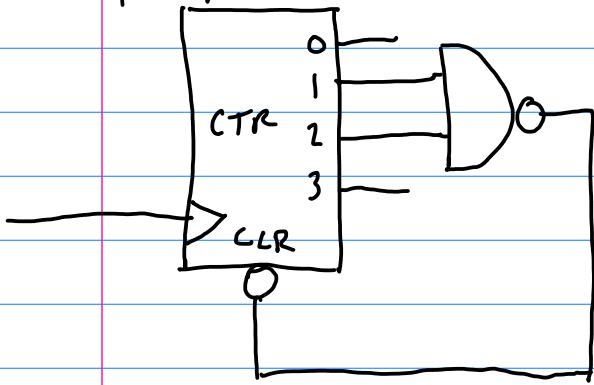

Synchronous

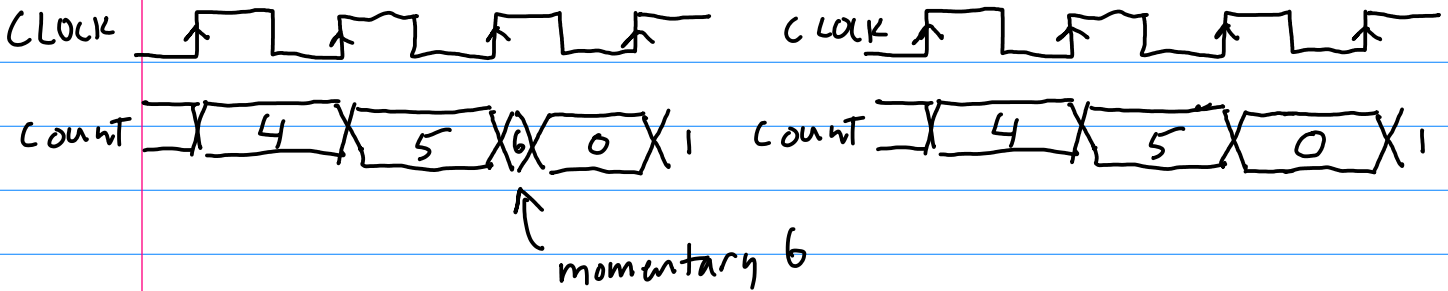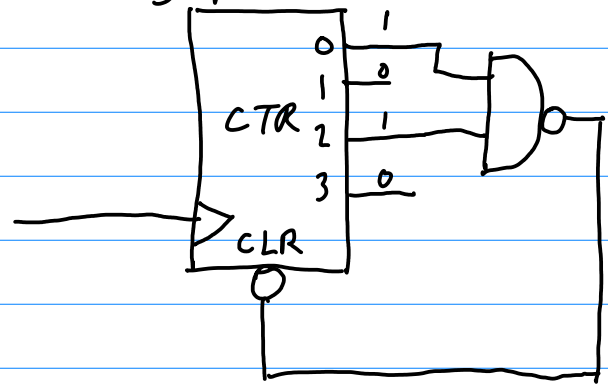



Cascade counters:

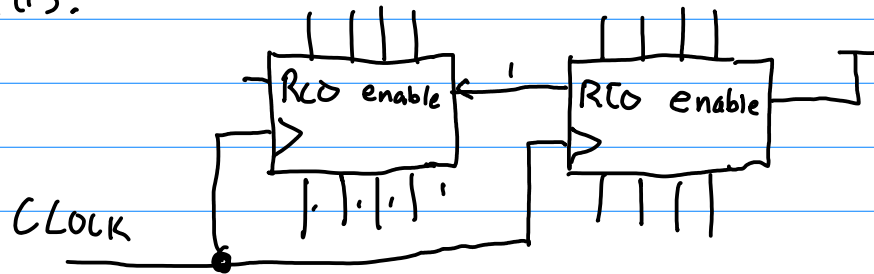


$\underline{RCO} = 1$ when count = $\underline{1111}$ AND $RCO_{EN} = 1$

e.g

Count 6 → 15

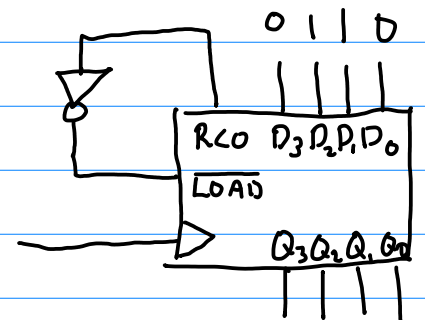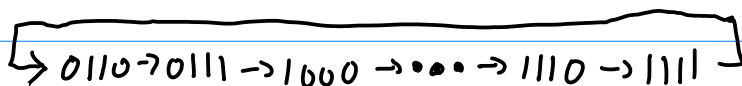

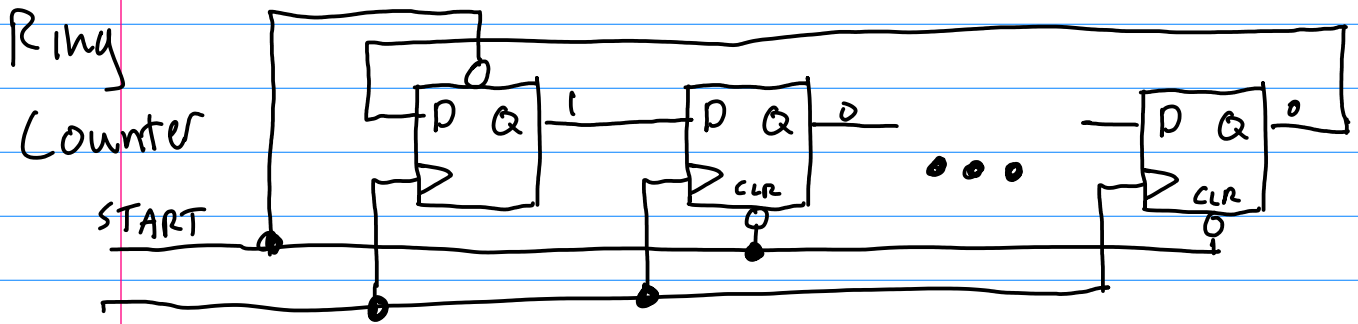Another shift register "One-hot" encoding




START will preload \rightarrow

1	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0
0	0	1	0	0	0	0	0
...
0	0	0	0	0	0	0	1

One-hot

Johnson Counter

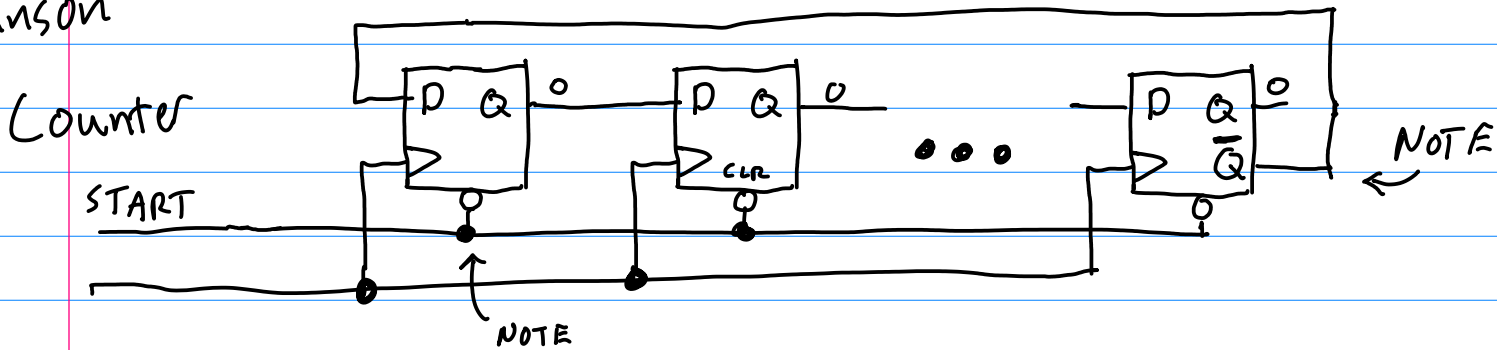

NOTE
Can use JK-ff for shift registers

Count \rightarrow

0	0	0	0
1	0	0	0
1	1	0	0
1	1	1	0
1	1	1	1
0	1	1	1
0	0	1	1
0	0	0	1